



**MAK-003-001502**

Seat No. \_\_\_\_\_

**B. Sc. (Sem. V) Examination**

**October / November – 2016**

**Physics : Paper - P - 502**

*(Electricity, Magnetism & Solid State Electronics)*

**Faculty Code : 003**

**Subject Code : 001502**

Time :  $2\frac{1}{2}$  Hours]

[Total Marks : 70

- Instructions :** (1) All the questions are compulsory.  
(2) Give answers of all questions in answer book only.  
(3) Figures on the right indicate full marks.

1 Answer following questions : **20**

(a) Match the following : **5**

- |                         |                                                        |
|-------------------------|--------------------------------------------------------|
| (i) Ampere's Law        | (a) $\nabla \times E = -\frac{\partial B}{\partial t}$ |
| (ii) Poisson's Equation | (b) $\nabla \cdot E = \frac{\rho}{\epsilon_0}$         |
| (iii) Gauss's Law       | (c) $\nabla \times B = \mu_0 J$                        |
| (iv) Laplace's Equation | (d) $\nabla \cdot E = -\frac{\rho}{\epsilon_0}$        |
| (v) Faraday's Law       | (e) $\nabla^2 V = 0$                                   |

(b) Fill in the blanks : **15**

- (1) In magnetostatics the continuity equation is given by \_\_\_\_\_.
- (2) A moving charge will gain energy due to the application of \_\_\_\_\_ field.
- (3) The primary source of energy is \_\_\_\_\_.

- (4) The calorific value of a solid fuel is expressed in \_\_\_\_\_ or \_\_\_\_\_.
- (5) \_\_\_\_\_ coal has highest calorific value.
- (6) The frequency response of \_\_\_\_\_ coupling is poor.
- (7) The frequency response of RC coupling is \_\_\_\_\_.
- (8) The ratio of a.c. output power to the zero signal power supplied by the battery of a power amplifier is known as \_\_\_\_\_.
- (9) The maximum collector efficiency of transformer coupled class A power amplifier is \_\_\_\_\_ %.
- (10) The variation of output voltage w.r.t. the amount of load current drawn from the power supply is known as \_\_\_\_\_.
- (11) \_\_\_\_\_ stage of a dc power supply uses a zener diode as the main component.
- (12) In \_\_\_\_\_ voltage regulator the regulated output voltage is equal to closed-loop voltage gains times the sum of zener voltage and base-emitter voltage.
- (13) In an electronic instrument \_\_\_\_\_ is used to convert the non-electrical quantity into the electrical quantity.
- (14) If two signals have the same frequency, then Lissajous figure shows \_\_\_\_\_ point of tangency along horizontal axis.
- (15) Analog instruments have \_\_\_\_\_ sensitivity than electronic instrument.

**2** (a) Answer any three questions :

**6**

- (1) What is hydroelectric power station?
- (2) Define an electric current.
- (3) What is an electrostatics?
- (4) State Maxwell's equations for electrostatics.
- (5) State Faraday's law in differential form.
- (6) Explain in brief generation of electrical energy.

- (b) Answer any **three** questions : **9**
- (1) Explain in brief divergence of B.
  - (2) Explain in brief curl of E.
  - (3) Explain the different terms of "work-energy theorem" of electrodynamics.
  - (4) Write a note on calorific value of fuels.
  - (5) State the advantages of liquid fuels over solid fuels.
  - (6) State advantages and disadvantages of hydroelectric power station.
- (c) Answer any **two** questions : **10**
- (1) Derive an expression for the work done to move a charge.
  - (2) State the different types of power stations and explain in brief any one.
  - (3) Explain an electric flux and derive an expression for Gauss law in differential form.
  - (4) Explain the term "magnetostatics" and "electrostatics".
  - (5) Discuss the advantages and disadvantages of nuclear power station.
- 3** (a) Answer any **three** questions : **6**
- (1) State advantages of transformer coupled transistor amplifier.
  - (2) Draw the circuit diagram of two stage transformer coupled transistor amplifier.
  - (3) Compare power and voltage amplifier.
  - (4) Derive an expression for collector efficiency.
  - (5) What is thermal runaway?
  - (6) What is voltage regulation?

(b) Answer any **three** questions : **9**

- (1) Explain with circuit diagram, an ordinary D.C. power supply.
- (2) State various types of voltage regulators.
- (3) Explain in brief frequency response of transformer coupled amplifier.
- (4) Write a short note on electron gun assembly in CRT.
- (5) State any nine applications of a CRO.
- (6) Write a short note on deflecting assembly in CRT.

(c) Answer any **two** questions : **10**

- (1) Explain the working of transformer coupled transistor amplifier with circuit diagram.
  - (2) Explain the working of RC coupled transistor amplifier with circuit diagram.
  - (3) Explain series feedback voltage regulator with circuit diagram.
  - (4) Explain frequency determination by using Lissajous figures.
  - (5) Explain direct coupled amplifier with circuit diagram.
-