



PB-003-001603

Seat No. _____

B. Sc. (Sem. VI) (CBCS) Examination

March / April - 2020

Physics : P-603

(Solid State Electronics)

Faculty Code : 003

Subject Code : 001603

Time : $2\frac{1}{2}$ Hours]

[Total Marks : **70**

Instructions :

- (1) All the questions are compulsory.
- (2) Give answer of all questions in answer book only.
- (3) Figures on the right indicate full marks.

1 Objective Questions : 20

- (1) If a d.c or constant input is applied to differentiating circuit, the output will be _____.
- (2) A transistor can be used as a switch by driving it back and forth between _____ and _____ regions.
- (3) When a transistor is driven to saturation, ideally the I_c _____ and $V_{ce} =$ _____.
- (4) A small portion of positive and negative half cycle of the signal can be removed with the help of _____ circuit.
- (5) The temperature sensing element thermistor has _____ temperature coefficient.
- (6) A DIAC is a _____ layer _____ junction device.
- (7) A DIAC - TRIAC built in the same chip is called a _____
- (8) An SCR is a _____ layer - junction device.
- (9) A device that convert energy in one form to energy in another form is known as _____.
- (10) A single-phase full wave fully controlled bridge uses _____ SCR.

(11) In OPAMP as an integrator, the feedback component is _____.

(12) Write full name of LASCR.

(13) A microphone is classified as an _____ transducer.

(14) A thermocouple is a _____ generating type transducer.

(15) A tourmaline crystal represents a _____ transducer.

(16) The value of gauge factor for _____ gauges is varies from 50 - 200.

(17) An ideal OP - AMP has _____ voltage gain.

(18) The outputs at any instant of time depend only on the inputs applied at that instant of time is known as _____ circuits.

(19) In D flip - flop D = high gives a _____ state.

(20) In order to implement an variable switching function, a multiplexer must have _____ inputs.

2 (a) Answer any three question : **6**

- (1) State the disadvantages of mechanical switch?
- (2) Draw circuit diagram for two-transistor analogy of an SCR.
- (3) Draw the V-I characteristics for the any two of the following thyristor
 - (a) SCR
 - (b) diac
 - (c) triac
 - (d) SCS
- (4) State the classification of ICs based on scale of integration.
- (5) State any two disadvantages of an IC.
- (6) What is transducer?

(b) Answer any three question : 9

- (1) Explain in brief integrating circuit.
- (2) Explain in brief multivibrator.
- (3) Explain in brief positive clippers.
- (4) Explain in brief an ideal OP - AMP.
- (5) Explain in brief classification of transducer.
- (6) Explain in brief multiplexer.

(c) Answer any two question : 10

- (1) Draw the V-I characteristic of an SCR and explain its working principle.
- (2) With a neat circuit diagram, explain working of an astable multivibrator.
- (3) Explain the working of an automatic street lighting circuit using LDR and SCR.
- (4) Explain JK flip flop with circuit diagram and truth table.
- (5) Explain the working of illumination control circuit using DIAC and TRIAC.

3 (a) Answer any three question : 6

- (1) What is clipper?
- (2) Draw the circuit diagram of transistor mono stable multivibrator.
- (3) Compare transistor and thyristor.
- (4) What is clamping?
- (5) What is choppers?
- (6) What is memory?

(b) Answer any three question : 9

- (1) Explain in brief fabrication of resistor and capacitor in ICs.
- (2) Explain with circuit diagram D flip flop.
- (3) Write a short note on various types of microphones.
- (4) Explain in brief fabrication of diode in ICs.
- (5) Write a short note on multiplexer.
- (b) Write a short note on piezoelectric transducer.

(c) Answer any two question : 10

- (1) Discuss classification of ICs by functions.
- (2) Explain the working of automatic street light circuit using thyristor.
- (3) With a neat circuit diagram, explain working of bistable multivibrator.
- (4) Explain capacitive pressure transducer with diagram.
- (5) Explain RS flip flop with circuit diagram and truth table.
