



Seat No. \_\_\_\_\_

**HP-003-1032003**

**B. C. A. (Sem. II) (CBCS) (W.E.F. 2016)  
Examination**

**April - 2023**

**Computer Organization & Architecture : CS-09  
(Old Course)**

**Faculty Code : 003  
Subject Code : 1032003**

Time :  $2\frac{1}{2}$  / Total Marks : **70**

**1 (a) Attempt the following : 4**

- (1) Which is the invertor gate of OR gate ?
- (2) SOP stands for \_\_\_\_\_.
- (3) T-flipflop can be easily constructed from JK flipflop.  
(True/False)
- (4) Is flipflop is a sequentially designed circuit ?

**(b) Attempt any one : 2**

- (1) What is combinational circuit ?
- (2) What is truth table ? Explain it with any example.

**(c) Attempt any one: 3**

- (1) Explain full adder.
- (2) Simplify this function using K-map.

$$F(w,x,y,z) = \sum (0,2,4,6,9,11,13, 15)$$

**(d) Attempt any one : 5**

- (1) Write note on different types of gates.
- (2) Write note on types of flip-flops.

**2 (a) Attempt the following : 4**

- (1) LSI stands for \_\_\_\_\_
- (2) Multiplexer is also known as \_\_\_\_\_
- (3) Asynchronous counter is also known as \_\_\_\_\_
- (4) If we construct 8 bits MUX, then how many selection lines are required ?

(b) Attempt any one : 2

- (1) Explain IC and its types in brief.
- (2) List out register's applications.

(c) Attempt any one : 3

- (1) Explain Multiplexer.
- (2) Explain Encoder.

(d) Attempt any one : 5

- (1) Explain  $3 \times 8$  decoder.
- (2) Draw and explain bi-directional shift register.

**3** (a) Attempt the following : 4

- (1) Base of Hexa-decimal number is \_\_\_\_\_.
- (2) Write 1's complement of 101011.
- (3) Binary Addition of  $1011 + 1001 =$  \_\_\_\_\_.
- (4) If number is positive, then sign bit will be \_\_\_\_\_.

(b) Attempt any one : 2

- (1) Multiply 101 by 11 in binary.
- (2) Divide 110111 by 101 in binary.

(c) Attempt any one : 3

- (1) Explain fixed point representation with example.
- (2) Explain parity bit and sign bit with example.

(d) Attempt any one : 5

- (1) Explain error detection code.
- (2) Explain floating point representation with example.

**4** (a) Attempt the following : 4

- (1) ALU stands for \_\_\_\_\_.
- (2) Control word is of \_\_\_\_\_ number of bits.
- (3) RPN stands for \_\_\_\_\_.
- (4) Full form of AC register.

(b) Attempt any one : 2

- (1) Explain Memory stack,
- (2) Explain any one example of Micro operation.

(c) Attempt any one : 3

- (1) Draw and explain block diagram of ALU.
- (2) Explain Register Stack.

(d) Attempt any one : 5

- (1) Write a note on general register organization.
- (2) What is interrupt ? Explain its types.

**5** (a) Attempt following : 4

- (1) IOP stands for \_\_\_\_\_
- (2) Full form of BR signal in DMA.
- (3) DMA stands for \_\_\_\_\_
- (4) Which register holds the number of words to be transferred in DMA ?

(b) Attempt any one : 2

- (1) What is input output interface ?
- (2) What is programmed I/O ?

(c) Attempt any one : 3

- (1) Note on types of memory buses.
- (2) Write note on IOP.

(d) Attempt any one: 5

- (1) Explain how DMA works in detail.
- (2) Write note on DMA transfer.

---