



Seat No. _____

HP-003-2032003

B. C. A. (Sem. II) (W.E.F. 2019) Examination

April - 2023

CS - 09 : Computer Organization & Architecture

Faculty Code : 003

Subject Code : 2032003

Time : $2\frac{1}{2}$ Hours / Total Marks : **70**

1	(a)	Give answer of following :	4
	(1)	J-k flipflop is universal flip flop. (True/false)	
	(2)	Flip flop can store _____ bit of information.	
	(3)	An inverter is called _____ gate.	
	(4)	NAND gate is complement of AND gate. (Yes/No)	
	(b)	Answer in brief : (any one)	2
	(1)	Explain and gate in detail.	
	(2)	Explain D flipflop.	
	(c)	Answer in detail : (any one)	3
	(1)	Why j-k flipflop in detail.	
	(2)	Explain de-Morgan theorem.	
	(d)	Write a note on following : (any one)	5
	(1)	Solve using k-map by sum of product $F(w,x,y,z) = (0,2,5,8,11)$	
	(2)	Solve using k-map with product of sum and don't care condition. $F(a,b,c,d) = (0,2,4,6,9,11,12,14) + d(3,7)$	
2	(a)	Give answer of following :	4
	(1)	Full form of VLSI.	
	(2)	Logic states is only _____ or 0.	
	(3)	An encoder has 2^n line and produce _____ output line.	
	(4)	What is decoder?	

(b) Answer in brief : (any **one**) 2

- (1) Explain integrated circuit.
- (2) Explain shift register.

(c) Answer in detail : (any **one**) 3

- (1) Explain encoder in detail.
- (2) Explain 2*4 decoder.

(d) Write a note on following : (any **one**) 5

- (1) Explain bi-directional shift register with parallel load.
- (2) Explain 4*1 line multiplexer.

3 (a) Give answer of following : 4

- (1) Solve using 1's complement 010101.
- (2) The collection of 8 bit is called ____ byte.
- (3) What is the work of program counter?
- (4) What is the work of stack pointer?

(b) Answer in brief : (any **one**) 2

- (1) Solve $010101 + 10101 + 110011$.
- (2) Solve $101010 - 11111$.

(c) Answer in detail : (any **one**) 3

- (1) Solve using 2's complement 111000110.
- (2) Solve $110001 * 11.11$.

(d) Write a note on following : (any **one**) 5

- (1) Explain floating point representation.
- (2) Explain error detection code in detail.

4 (a) Give answer of following : 4

- (1) Full form of CPU.
- (2) Full form of RPN.
- (3) _____ number of bit used to perform complete operation.
- (4) _____ of bit needed to perform mathematical operation.

(b) Answer in brief : (any **one**) 2

- (1) Explain control word.
- (2) Explain RPN.

(c) Answer in detail : (any **one**) 3

- (1) Solve using RPN $A * B + C * D + E * F$.
- (2) Explain interrupts.

(d) Write a note on following : (any **one**) 5

- (1) Explain memory stack in detail.
- (2) Explain push and pop operation using stack.

5 (a) Give answer of following : 4

- (1) Full form of DMA.
- (2) What is data bus?
- (3) What is address bus?
- (4) What is control line?

(b) Answer in brief : (any **one**) 2

- (1) Define DMA.
- (2) Explain input output buses in detail.

(c) Answer in detail : (any **one**) 3

- (1) Explain input output interface.
- (2) Explain DMA transfer.

(d) Write a note on following : (any **one**) 5

- (1) Explain DMA controller.
- (2) Explain IOP.
