



Seat No. _____

HP-003-3032003

B. C. A. (Sem. II) (CBCS) (W.E.F.-2022) Examination
April – 2023

Computer Organization & Architecture : CS-09
(New Course)

Faculty Code : 003
Subject Code : 3032003

Time : $2\frac{1}{2}$ Hours / Total Marks : **70**

1	(a) Attempt the following :	4
	(1) Which is the inverter gate of LAND gate ?	
	(2) Is flip-flop is a sequentially designed circuit ?	
	(3) POS stands for.	
	(4) Write two commutative postulates.	
	(b) Attempt any one :	2
	(1) What is Boolean algebra ?	
	(2) What is combinational circuit ?	
	(c) Attempt any one :	3
	(1) Explain and prove De-Morgan's theorems.	
	(2) Simplify following Boolean function using K-map.	
	$F(w,x,y,z) = \sum(0,1,2,3,7,8,10) + d(5,6,11,15)$	
	(d) Attempt any one :	5
	(1) Write a detailed note on types of logic gates.	
	(2) Draw circuit and explain D and JK flip-flop.	

2 (a) Attempt the following : 4

- (1) What is Bi-directional shift register ?
- (2) De-Multiplexer is also known as _____.
- (3) If we construct 8 bits Mux, then how many selection lines are required?
- (4) VLSI stands for _____.

(b) Attempt any one : 2

- (1) Explain Buffer register.
- (2) Explain shift register.

(c) Attempt any one: 3

- (1) Write a note on 3x8 decoder.
- (2) Write a note on encoder.

(d) Attempt any one : 5

- (1) Explain multiplexer in detail.
- (2) Draw and explain register with parallel load.

3 (a) Attempt the following : 4

- (1) What is parity bit ?
- (2) Base of an octal number is _____
- (3) If number is negative, then sign bit will be _____.
- (4) Write 2's complement of 010011000.

(b) Attempt any one : 2

- (1) Perform binary multiplication of 1011×101 .
- (2) Perform binary division of $110111 \div 101$.

(c) Attempt any one : 3

- (1) Multiply 1011.01 by 101.01 in binary.
- (2) Explain fixed point representation with example.

(d) Attempt any one : 5

- (1) Explain floating point representation with example.
- (2) Explain error detection code with example.

4 (a) Attempt following : 4

- (1) CPU stands for _____.
- (2) (A+B) * C write prefix notation of given expression.
- (3) Control word is of _____ number of bits.
- (4) Register overflow is an example of _____ type of interrupt.

(b) Attempt any one : 2

- (1) Explain major components of CPU.
- (2) Explain Register Stack.

(c) Attempt any one : 3

- (1) Explain interrupt and its various types.
- (2) Draw and explain block diagram of A.L.U.

(d) Attempt any one : 5

- (1) Write a note on general register organization.
- (2) Write a detailed note on RPN with stack organization.

5 (a) Attempt following : 4

- (1) IOP stands for _____.
- (2) DMA stands for _____.
- (3) List out memory buses.
- (4) Full form of BG signal in DMA.

(b) Attempt any one : 2

- (1) What is high impedance model ?
- (2) Write concept of input output interface.

(c) Attempt any one : 3

- (1) Explain memory buses.
- (2) Explain how DMA works in brief.

(d) Attempt any one : 5

- (1) Write a detailed note on DMA controller.
- (2) Write a detailed note on IOP.