



DB-003-001603

Seat No. _____

B. Sc. (Sem. VI) (C.B.C.S.) Examination

April / May – 2015

Physics

Faculty Code : 003

Subject Code : 001603

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (i) All questions are compulsory.
(ii) Figures on the right side indicate marks.
(iii) Symbols have their usual meaning.

1 Select the correct answer from the given options : **20**

(1) When a transistor is driven to saturation, ideally the output is _____.

- (A) V_{CC} (B) 0
(C) $V_{CC}/2$ (D) $2V_{CC}$

(2) _____ multivibrator is a square wave oscillator.

- (A) Monostable (B) Astable
(C) Bistable (D) None of these

(3) If 10 V dc is supplied to the input of differential circuit, its output will be _____.

- (A) 20 V (B) 10 V
(C) 0 V (D) None of the above

(4) For the integrating circuit, the capacitive reactance X_C , should be _____ than the resistance R.

- (A) 10 times greater (B) 10 times smaller
(C) 5 times smaller (D) 5 times greater

(5) Which relation is correct for SCR anode current ?

(A) $I_A = \left[\frac{\alpha_2 I_g}{1 + (\alpha_1 + \alpha_2)} \right]$ (B) $I_A = \left[\frac{\alpha_1 I_g}{1 - (\alpha_1 + \alpha_2)} \right]$

(C) $I_A = \left[\frac{\alpha_2 I_g}{1 - (\alpha_1 + \alpha_2)} \right]$ (D) None of these

(6) Which of these is not a Thyristor ?

- (A) LASCR (B) LASCS
(C) SBS (D) LDR

(7) A TRIAC behaves like _____.

- (A) two inverse parallel SCRs with common gate
(B) four layer diodes in parallel
(C) two inverse parallel diodes
(D) two transistors with base of one connected to collector of another.

- (8) A TIRAC can be triggered into conduction by ____.
- (A) only positive voltage at either anode
 - (B) positive or negative voltage at either anode
 - (C) positive or negative voltage at either gate
 - (D) both (B) and (C)
- (9) The angle at which the device is triggered is known as ____.
- (A) phase angle
 - (B) firing angle
 - (C) conduction angle
 - (D) infinite
- (10) Which of these thyristor is bidirectional ?
- (A) SCR
 - (B) SCS
 - (C) LASCR
 - (D) DIAC
- (11) ____ cannot fabricated in monolithic IC.
- (A) Capacitor
 - (B) Resistor
 - (C) Diode
 - (D) Inductor
- (12) Isolation in monolithic IC is ____.
- (A) Good
 - (B) Excellent
 - (C) Poor
 - (D) Very poor
- (13) Basically Op-Amp is designed to perform the ____.
- (A) Logic operation
 - (B) Analog operation
 - (C) Mathematical operation
 - (D) Digital operation

- (14) In monolithic IC capacitor, the SiO_2 acts as ____.
- (A) positive plate
 (B) negative plate
 (C) dielectric medium
 (D) either (A) or (B)
- (15) A microphone is classified as a ____ transducer.
- (A) thermal (B) optical
 (C) magnetic (D) acoustical
- (16) Strain gauge with gauge factor 2, no strain resistance $120\ \Omega$ and it is subjected to strain of order 10^{-6} . The fractional change in resistance is ____.
- (A) $240\ m\Omega$
 (B) $240\ \Omega$
 (C) $240\ \mu\Omega$
 (D) Either (A) or (C)
- (17) Strain gauge with gauge factor 2, and modulus of elasticity $21 \times 10^{12}\ N/m^2$, no strain resistance $120\ \Omega$ and it is subjected to stress of about $10.5 \times 10^9\ N/m^2$. Strain produced in gauge is ____.
- (A) 50×10^{-4} (B) 5×10^{-4}
 (C) 5×10^{-6} (D) 50×10^{-6}

(b) Answer any three : 9

- (1) What is differentiating circuit ? Draw circuit diagram and prove the relation between output and input voltage.
- (2) What is clipping circuit ? Explain biased clipper.
- (3) Give the basic idea of the clamping circuit.
- (4) Write applications of thyristor.
- (5) Explain structure and operation of DIAC.
- (6) Explain 'Off at dark' circuit.

(c) Answer any two : 10

- (1) Explain transistor free running multivibrator.
- (2) Explain the I-V characteristic of an SCR.
- (3) Explain integrating circuit.
- (4) Explain working of an Automatic street light circuit using SCR and LDR.

3 (a) Answer any three : 6

- (1) What is an integrated circuit ?
- (2) Classify ICs based on scale of integration.
- (3) What is transducer ? Explain it.
- (4) Explain working of electrical transducer.
- (5) Draw logic diagram of basic RS flip-flop and realize the truth table.
- (6) Draw logic diagram and give truth table of JK flip-flop.

(b) Answer the three : 9

- (1) What is an Op-Amp ? Explain.
- (2) Explain OP-Amp as Adder.
- (3) Write a note on thin film IC.
- (4) Explain strain gauge.
- (5) Discuss basic RS flip-flop.
- (6) Discuss D-flip-flop.

(c) Answer any two : 10

- (1) Explain use of Op-Amp as inverting amplifier.
- (2) Describe the fabrication of monolithic IC.
- (3) Explain constructive and working of LVDT.
- (4) Write a note on classification of transducer.
- (5) Write a note on multiplexer and demultiplexer.
