



HCU-003-1273001 Seat No. _____

M. Sc. (ECI) (Sem. III) (CBCS) Examination

October / November - 2017

Paper - IX : Advance Circuit & Network Concepts

Faculty Code : 003


Subject Code : 1273001

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

1 Answer any seven from the following : 14

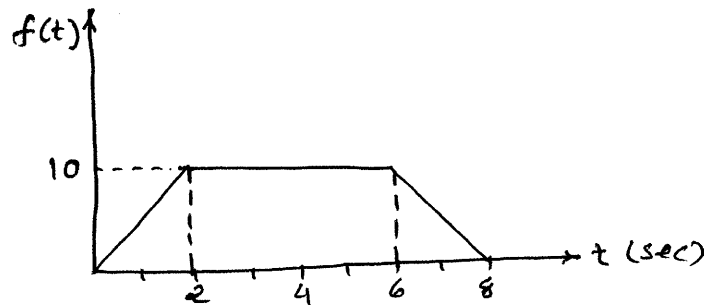- (1) Use step function to write the expression for the following function :



- (2) Find the Laplace transform of the function,

$$f(t) = 4t^3 + t^2 - 6t + 7$$

- (3) Find Laplace transform of $\sin 3t$. Use derivative formula.

- (4) Determine the partial fraction expansion for,

$$F(S) = \frac{S-5}{S(S+2)^2}$$


- (5) Verify the initial value theorem for following function.

$$f(t) = 2 - e^{5t}$$

- (6) Verify the final value theorem for the following function.

$$f(t) = 2 + e^{-3t} \cos 2t$$

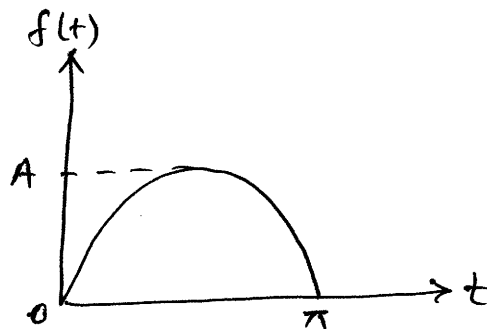- (7) Write the expression for following waveform in terms of unit function. Then obtain the Laplace transform for the same.



- (8) Determine the Laplace transform of $\frac{d^2y}{dt^2}$ if $y = t^2$.
- (9) Determine partial fraction expansion for the following.

$$F(S) = \frac{S-1}{(S+9)^2(S+4)(S^2+3S+2)(S+7)^2}$$

- (10) Determine the inverse Laplace of following.

$$F(S) = \frac{96(S+5)(S+12)}{S(S+8)(S+6)}$$

2 Answer any two from the following :

- (a) Discuss the natural response of an RC circuit using S - domain analysis. 7
- (b) Discuss the response of a circuit where input generates Impulse source by switching a capacitor. 7
- (c) Discuss transform impedance of capacitor. 7

3 Answer the following :


- (a) Explain following statements for pole and zero concepts : 7
- (1) "The real parts of all zeros and poles must be negative or zero".
- (2) "Poles and zeros lying on the $j\omega$ - axis must be simple".

- (b) A network function has two real poles. Discuss its time response using pole zero concept. If the same function has two complex poles, discuss its time response. 7

OR

3 Answer the following :

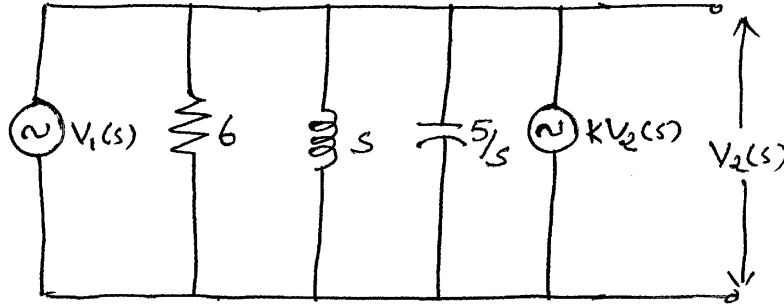- (a) Discuss the stability criterion for the following active network in S-domain. 7



- (b) Represent ABCD parameters in terms of Z-parameters and Y-parameters. 7

4 Answer the following :

- (a) For T-network filter prove the following : 7

$$(1) \quad Z_{0T} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$(2) \quad Z_{0T} = \sqrt{Z_{0c} * Z_{sc}}$$

$$(3) \quad \gamma = \ln \left[1 + \frac{Z_1}{2Z_2} + \sqrt{\left(\frac{Z_1}{2Z_2} \right)^2 + \frac{Z_1}{Z_2}} \right]$$

- (b) What are the limitations of constant k filter ? Discuss m-derived low pass filter. 7

5 Answer any two from the following :

- (a) Draw and explain full shunt equalizer. 7

- (b) Discuss the realization of immittance function of LC network given below for Foster-I and Cauer-I form 7

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- (c) Realize the following RC network impedance function for Foster-II and Cauer-II methods : 7

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)}$$

- (d) Explain the basics of synthesis of driving point impedance function of RL networks. Write the properties of RL driving point impedance function. Write about the plot of $Z(\sigma) \rightarrow \sigma$. 7
-