



HEG-16030102010200 Seat No. _____

M. Sc. (Physics) (CBCS) (Sem. I) Examination

November/December – 2017

CT-02 : Solid State Electronic Devices & Circuits

(New Course)

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Figures on the right hand side indicate marks.

1 Answer the following : (any seven) **14**

- (a) Draw transfer characteristic of JFET. Define : Transconductance.
- (b) Show that dual and complement of Boolean expression of 2-input exclusive OR gate are same.
- (c) Which one is the fastest logic family ?
- (d) Distinguish between direct and indirect band gap materials.
- (e) Calculate transconductance (g_m) of JFET having the parameters : $I_{DSS} = 16\text{ mA}$, $V_p = -4\text{ V}$ for drain current $I_D = 1\text{ mA}$.
- (f) Calculate wavelength (λ_g) of light emission for GaP having band gap energy $E_g = 2.26\text{ eV}$.
- (g) Prove that product of all the Maxterms of a Boolean function of N-variable is 0.
- (h) How many Lumens make one watt of radiant energy ?
- (i) What is the operational principle of Solar cell ?
- (j) Simplify the following Boolean function :
$$F = (A + B)' \cdot (A' + B')$$

- 2 Answer the following : (any two) 14
- (1) Compare : BJT and JFET. Describe the construction of N-channel JFET and explain its drain-source characteristics.
 - (2) Discuss various DC biasing methods for JFET with neat diagrams. What is the advantage of self biasing over fixed biasing ?
 - (e) Write a detailed note on various types of MOSFETs.

- 3 Answer the following : 14
- (a) Draw the circuit of 2-input NAND gate using transistor-transistor logic and explain its operation in detail.
 - (b) Prepare truth table for the Boolean function :

$$F = A + B' \cdot C.$$

OR

- 3 Answer the following : 14
- (a) A logic circuit having three inputs should produce high output when its input binary number has majority of bits high. Design the logic circuit using K-Map and draw the circuit using AND-OR implementation.
 - (b) Simplify the following Boolean function using Karnaugh method :

$$F(w, x, y, z) = \sum (3, 6, 7, 11, 14, 15).$$

$$\text{And don't cares are : } d(w, x, y, z) = \sum (0, 2, 10).$$

- 4 Answer the following : (any two) 14
- (a) What are thyristors ? Enumerate various types of thyristors. Draw basic structure and symbol of Silicon Controlled Rectifier. Explain the current voltage characteristics of SCR and derive anode current expression for forward blocking state.
 - (b) What is meant by direct band gap and indirect band gap semiconductors ? Explain the physics of light emission in LED. Give a brief note on LED materials.
 - (c) Discuss in detail the physics of photoconductive detectors hence derive expression for photoconductive gain. What are the photoconductive materials ?

5 Write short notes on any two :

14

- (a) Solar cell : Principle, structure and characteristics
 - (b) Thermistors and applications
 - (c) Zener diode voltage regulator
 - (d) Uni-junction transistor and UJT relaxation oscillator.
-