



NCF-003-0492006 Seat No. _____

**B. Sc. / M. Sc. (Applied Physics) (Integrated)
(Sem. II) (CBCS) Examination**

April / May - 2017

**Basic Electronics : Paper - VIII
(New Course)**

Faculty Code : 003

Subject Code : 0492006

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Symbols have their usual meaning.
(3) Figures on right side indicate full marks.

1 Attempt any **seven** short questions : (two marks each) **14**

- (1) What is a Zener diode? Draw V - I characteristics of Zener diode.
- (2) Which are the most commonly used semiconductors and why?
- (3) Give the names of most commonly used filter circuits.
- (4) Give the name of device which works as a voltage controlled capacitance.
- (5) Draw the common base and common collector connections.
- (6) What is transistor? Explain the construction of transistor.
- (7) What is faithful amplification?
- (8) Write the advantages of transistor.
- (9) Write essentials for a biasing circuit.
- (10) Discuss the stabilization of operating point.

- 2** Write answers of following questions : **14**
- (a) (1) Draw the symbol of crystal diode and Zener diode. **2**
- (2) What is the breakdown voltages for Ge and Si. **2**
- (b) Explain intrinsic and extrinsic semiconductors. **5**
- (c) What is a ripple factor? Calculate value for a half wave and full wave rectifier. **5**

OR

- 2** Write answers of following questions : **14**
- (a) (1) Draw the symbol of crystal diode and Zener diode. **2**
- (2) What is crystal diode? Explain its rectifying action. **2**
- (b) Explain working of Full wave bridge rectifier with neat sketch. **5**
- (c) What is a PN junction? Explain the formation of potential barrier in PN junction. **5**

- 3** Write answers of following questions : **14**
- (a) (1) Draw symbols of LED, Photodiode, Varactor and Shockley diode. **2**
- (2) Why photodiode is connected in reverse bias? **2**
- (b) Discuss tunnel diode and explain V-I characteristics of tunnel diode. **5**
- (c) Explain the working of Photo diode with its applications. **5**

OR

- 3** Write answers of following questions : **14**
- (a) (1) How LED differs from an ordinary diode? **2**
- (2) What is an optoisolator? **2**
- (b) Explain the working of Shockley diode. **5**
- (c) Explain the working of varactor diode with its applications. **5**

- 4 Write answers of following questions : 14
- (a) (1) What do you understand by d.c. and a.c. load lines? 2
- (2) Draw the symbol of NPN and PNP transistor. 2
- (b) Discuss input and output characteristics of common collector connection of transistor. 5
- (c) Compare the various characteristics of CE, CB and CC connections in transistor. 5

OR

- 4 Write answers of following questions : 14
- (a) (1) Write the mathematical relation between β and α . 2
- (2) Explain voltage gain in transistor. 2
- (b) Discuss input and output characteristics of common emitter connection of transistor. 5
- (c) Write short notes on : 5
- (1) Advantages of transistor and
- (2) Operating point.

- 5 Write answers of following questions : 14
- (a) (1) Give the names of different audio power amplifiers. 2
- (2) What is an audio power amplifier? What is its need? 2
- (b) Compare the RC coupling, Transformer Coupling and Direct Coupling. 5
- (c) Describe potential divider in detail. How stabilization of operating point is achieved by this method? 5

OR

- 5 Write answers of following questions : 14
- (a) (1) Draw the block diagram of multistage transistor amplifier. 2
- (2) What is the disadvantage of voltage divider biasing? 2
- (b) Discuss RC coupled transistor amplifier. 5
- (c) Give the names of various methods used for transistor biasing. Discuss any one method with its advantages and disadvantages. 5
-