



**NBH-003-1042003** Seat No. \_\_\_\_\_

**B. Sc. (I.T.) (Sem. II) (CBCS) Examination**

**April / May - 2017**

**CS-09 : Computer Organization & Architecture**

*(New Course)*

**Faculty Code : 003**

**Subject Code : 1042003**

Time :  $2\frac{1}{2}$  Hours]

[Total Marks : 70

- 1 (a) Attempt Following Question : 4
- (1) Which gate is Known as Universal Gate?
  - (2) Flip Flop store how many bits?
  - (3) State True or False :  
Master Slave Flip Flop is constructed using JK FF?
  - (4) In JK flip flop, JK stands for ?
- (b) Attempt following question : (any one) 2
- (1) Draw circuit of boolean equation  $A+A'B$ .
  - (2) Give the simplification of  $AB+AB'$ .
- (c) Attempt Following Question : (any one) 3
- (1) Explain half Adder.
  - (2) Simplified the equation using k-map.  
 $F(W, X, Y, Z) = \Sigma(0, 2, 4, 6, 9, 11, 13, 15)$
- (d) Attempt Following Question : (any One) 5
- (1) What is Logic Gates? Explain Basic Gates in detail.
  - (2) Explain S-R flip flop in detail.

- 2 (a) Attempt following question : 4
- (1) In Shift Register which Flip flop is used ?
  - (2) 3 to 8 line Decoder is also called \_\_\_\_\_ Decoder?
  - (3) What is IC ?
  - (4) What is Multiplexer?
- (b) Attempt following question : (any one) 2
- (1) What is Register? List out all types of Register.
  - (2) Write down the application of Multiplexer.
- (c) Attempt following question : (any one) 3
- (1) Explain Buffer register in detail..
  - (2) Explain Octal - To - Binary Encoder in detail.
- (d) Attempt following question : (any one) 5
- (1) Explain 3 to 8 line Decoder in detail.
  - (2) Explain Bi-directional shift register with parallel load.
- 3 (a) Attempt following question : 4
- (1) Perform 1's complement of 101001010?
  - (2) In signed Magnitude representation system, Orepresent \_\_\_\_\_ number?
  - (3) The decimal equivalent of binary number 10101 is \_\_\_\_\_ ?
  - (4) What is Error Detection Code?
- (b) Attempt Following question : (any one) 2
- (1) Perform  $1101 * 110$ .
  - (2) Perform  $1010 / 101$ .
- (c) Attempt following question : (any one) 3
- (1) Explain Term Overflow, Underflow, Normalization.
  - (2) Explain 2's Complement method in detail with example.

- (d) Attempt Following question : (any **one**) 5
- (1) What is Parity Bit? Explain P(odd) and P(even) in detail.
  - (2) Explain floating point representation number system in detail.
- 4 (a) Attempt following question : 4
- (1) Stack Works on \_\_\_\_\_ algorithm.
  - (2) How many control word in General Register Organization?
  - (3) \_\_\_\_\_ register is multipurpose register.
  - (4) In prefix notation the operator is placed \_\_\_\_\_ the operand.
- (b) Attempt following question : (any **one**) 2
- (1) Convert expression into prefix Notation.  
(A+B) / (C-D)
  - (2) Write a POP operation algorithm of stack.
- (c) Attempt following question : (any **one**) 3
- (1) Write a short note on ALU.
  - (2) What is Interrupt explain in detail with types.
- (d) Attempt Following question : (any **one**) 5
- (1) Explain General Register Organization in detail.
  - (2) Explain Stack Organization in detail.
- 5 (a) Attempt following question : 4
- (1) In most of computer CPU is \_\_\_\_\_ and IOP is \_\_\_\_\_.
  - (2) BG stands for ?
  - (3) In IOP computer is divide into \_\_\_\_\_ module(Parts)?
  - (4) State true or false. RD(read) and WR(write) lines are bi-directional.

- (b) Attempt following question : (any **one**) **2**
- (1) Explain term Burst Transfer, Cycle Stealing.
  - (2) Explain Programmed input-output.
- (c) Attempt following question : (any **one**) **3**
- (1) Explain IOP in detail.
  - (2) Explain Address register , Word - count Register and Control Register in detail.
- (d) Attempt following question : (any **one**) **5**
- (1) Explain DMA Transfer in detail.
  - (2) Explain DMA controller in detail.
-