



NCC-003-1272002 Seat No. _____

M. Sc. (ECI) (Sem. II) (CBCS) Examination

April / May - 2017

Advanced Digital Electronics : Paper - VI

Faculty Code : 003

Subject Code : 1272002

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

1 Answer the following questions in brief. : (any seven) **14**

- (1) Explain working of RS Flip-Flop as key de-bouncer.
- (2) Explain in brief synchronous and asynchronous inputs to Flip-Flop.
- (3) What is multivibrator? Define various types of multivibrators.
- (4) Explain modules of counter.
- (5) Draw the diagram of ring counter and explain in brief.
- (6) Compare asynchronous counter with synchronous counter.
- (7) Enlist types of Analog to Digital converters.
- (8) Define resolution and conversion time for an Analog to Digital converter.
- (9) Enlist various types of programmable logic devices.
- (10) Compare fixed logic to programmable logic.

2 Attempt any **two** of the following questions : **14**
(Each 7 marks)

- (1) Enlist and explain various timing parameters of Flip-Flop.
- (2) Enlist various types of shift register. Explain working of any two types of shift register with help of necessary diagrams.
- (3) With help of neat diagrams explain both types of Digital to Analog Converter.

- 3** Answer the following questions :
- (1) Describe programmable Logic Array (PLA) architecture. **5**
 - (2) Design a mod-6 asynchronous counter and explain its working with help of neat diagram. **5**
 - (3) Write a detailed note on JK flip-flop. **4**

OR

- 3** Answer the following questions :
- (1) How counters can be cascaded? Explain with suitable example. **5**
 - (2) With neat diagram explain the working of a 4-bit shift counter. **5**
 - (3) Write a detailed note on various programmable interconnect technologies. **4**

- 4** Answer the following questions :
- (1) With necessary diagrams explain flash type Analog to Digital converter. **5**
 - (2) Write a note on monostable multivibrator. **5**
 - (3) Explain working of 3-bit binary asynchronous counter with help of neat diagram. **4**

- 5** Answer any **two** of the following questions. (Each 7 marks) **14**
- (1) Write a detailed note on D latch, Also explain edge triggering.
 - (2) With help of neat diagrams explain working of 3-bit binary synchronous counter.
 - (3) With help of neat diagrams explain successive Approximation type Analog to Digital converter.
 - (4) Give a detailed account on complex programmable Logic Devices (CPLD) architecture.