



\* N B R - 0 0 3 - 0 2 7 8 0 4 \*

**NBR-003-027804**

Seat No. \_\_\_\_\_

**M. Sc. (ECI) (Sem. VIII) (CBCS) Examination**

**April / May - 2017**

**Paper - 32 : VHDL : Fundamentals & Practice  
(New Course)**

**Faculty Code : 003**

**Subject Code : 027804**

Time :  $2\frac{1}{2}$  Hours]

[Total Marks : 70

**Instructions :**

- (1) All questions carry equal compulsory.
- (2) Figures on right hand side indicate marks.

**1 Answer the following : (any seven) 14**

- (1) What is VHDL ?
- (2) Write about Library declaration in VHDL.
- (3) Write the syntax of "ARCHITECTURE" of VHDL code.
- (4) Make a list of Pre-defined data types of VHDL.
- (5) Define. Array in VHDL.
- (6) Define d'RIGHT and d'LENGTH data attributes of VHDL.
- (7) What is sequential logic in VHDL ?
- (8) Define PROCESS section of VHDL code.
- (9) Write difference between Signal and Variable of VHDL.
- (10) What is state machine ?


**2 Answer the following : (any two) 14**

- (1) Explain fundamental VHDL units and design flow of VHDL. 7
- (2) Write a VHDL code for' Multiplexer. 7
- (3) Write a VHDL code of 4-bit Adder with one output (sum) for both SIGNED and INTEGER datatypes. 7

- 3** Answer the following : **14**
- (1) Explain STD\_LOGIC, STD\_ULOGIC, BOOLEAN, INTEGER, SIGNED, UNSIGNED data types of VHDL. **7**
- (2) Explain Assignment, Logical and Shift operators of VHDL. **7**

**OR**

- 3** Answer the following : **14**
- (1) Write a note on combinational versus sequential logic. **7**
- (2) Explain GENERATE statement with example. **7**
- 4** Answer the following : **14**
- (1) Write a VHDL program for 1-digit decimal counter (0 → 9 → 0), according to top-level diagram shown in **fig. (a)**. **7**

 

**Fig. (a)**

- (2) Explain FOR/LOOP, WHILE/LOOP, NEXT, EXIT with examples. **7**
- 5** Answer the following : (any two) **14**
- (1) Write a VHDL code for D-Flip-flop with output Q and Qbar. **7**
- (2) Explain Mealy State Machine with diagram. **7**
- (3) Write a VHDL program for GENERIC 3:8 Decoder. **7**
- (4) Write a VHDL program for Encoder. **7**