



NCD-003-027202 Seat No. _____

**M. Sc. (Electronics, Computer & Instrumentation)
(Sem. II) (CBCS) Examination**

April / May - 2017

Basic Circuit Analysis : Paper - 6

Faculty Code : 003


Subject Code : 027202

Time : $2\frac{1}{2}$ Hours]


[Total Marks : 70

1 Answer the following : (Any Seven) 14

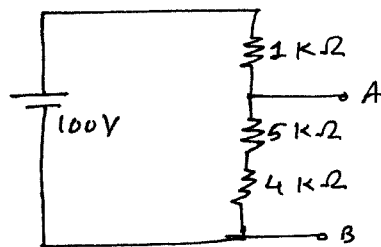- (1) Define Voltage and Current.
- (2) What are the bilateral and unilateral elements? Give examples.
- (3) Prove that for inductor $i(t) = \frac{1}{L} \int_0^t v dt + i(0)$.
- (4) Find the voltage between A and B for the following circuit.



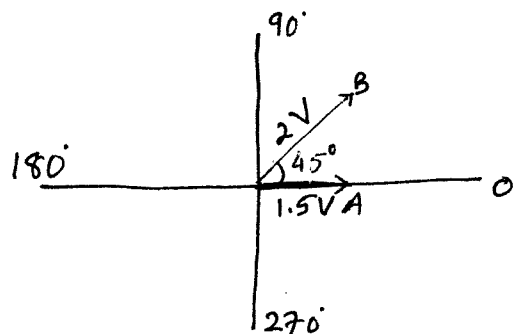
- (5) Define tree, co-tree, twig and link.
- (6) Write the condition for any network to become "supermesh" and "supernode".
- (7) State Thevenin and Norton theorems.
- (8) Prove the $v_{av} = 0.637v_p$ for sine wave.
- (9) Draw the waveform from the following phasor diagram,




- (10) Determine the average power, P_{av} , delivered to the circuit consisting of an impedance $Z = 5 + j8$ when current flowing through the circuit is $I = 5\angle 30^\circ$.

2 Answer any two from the following :

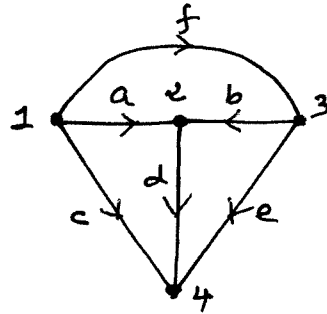- (1) Write the Kirchhoff's current law. Explain current division rule. 7
- (2) Draw all possible trees for the following graph : 7




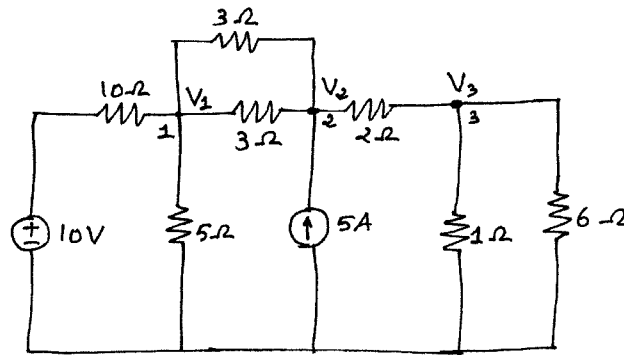- (3) Determine the voltage at each node for the circuit shown below : 7



3 Answer the following :

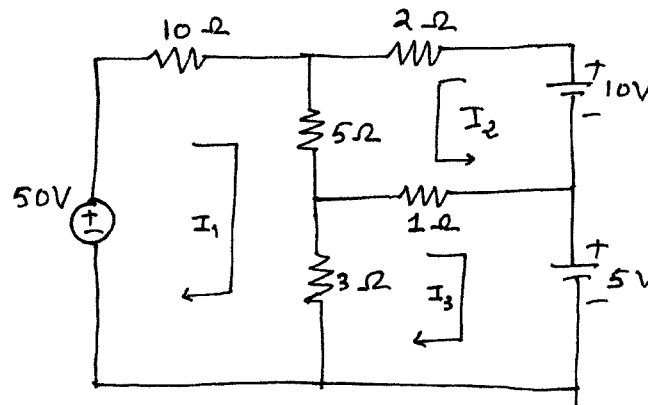- (1) Determine mesh currents I_1, I_2 and I_3 in the following circuit. 7




- (2) Draw star and delta network. Prove that 7

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3}, R_B = \frac{R_1 R_3}{R_1 + R_2 + R_3} \text{ and } R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$


Where R_A, R_B and R_C are resistances of star network and R_1, R_2 and R_3 are resistances of delta network.

OR


- 3 Answer the following :
- (1) Explain superposition theorem with one example. 7
- (2) Explain duals and duality with one example. 7
- 4 Answer any **two** from the following :
- (1) Explain following for sine wave 7
- (A) Phase of sine wave
- (B) RMS value
- (C) Peak value
- (D) Form factor
- (2) Discuss series RLC circuit in terms of its phase relation of V_R, V_L and V_C and Impedance. 7
- (3) Explain the following with necessary mathematical steps. 7
- (A) Average power
- (B) Apparent power.
- 5 Answer any **two** from the following :
- (1) For the circuit shown below, determine the current in $(2 + j3)$ ohm by using the superposition theorem. 7

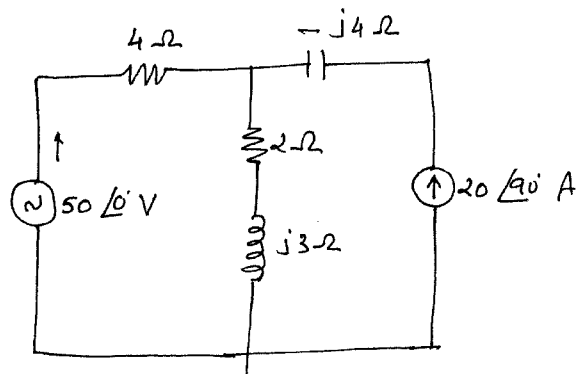

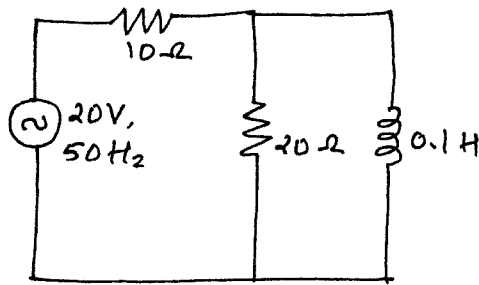- (2) For the circuit shown below find X_L , Z_T , I_T and θ . 7



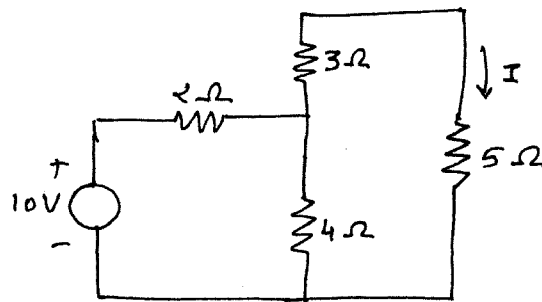- (3) Verify the reciprocity theorem for the following circuit. 7



- (4) For following circuit find the power delivered by 4V source using mesh analysis and voltage across the 2 ohm resistor. 7

