



**HAF-003-001603**

Seat No. \_\_\_\_\_

**B. Sc. (Sem. VI) (CBCS) Examination**

**June / July - 2017**

**Physics : Paper - 603  
(Solid State Electronics)**

**Faculty Code : 003**

**Subject Code : 001603**

Time :  $2\frac{1}{2}$  Hours ]

[ Total Marks : 70

- Instructions :** (1) Attempt all the questions.  
(2) Figures on right side indicate marks.

**1** All questions are compulsory : **20**

- (1) Bistable multivibrator has \_\_\_\_\_ stable state.
- (2) If the input to a differentiating circuit is a saw-tooth wave then the o/p will be \_\_\_\_\_ wave.
- (3) Draw the circuit diagram of integrating circuit.
- (4) How many PN junctions has SCR?
- (5) How many PN layers has Triac ?
- (6) Which terminal is used for control in an SCR ?
- (7) DIAC conduct in \_\_\_\_\_ direction.
- (8) Give the full name of LASCR.
- (9) Which ICs are the most commonly used ?
- (10) Which passive element can not be fabricated on an IC ?
- (11) The input resistance  $R_i =$  \_\_\_\_\_ of an Op-Amp.
- (12) Give any two applications of Op-Amp.
- (13) What is called transducers ?
- (14) Strain gauge is a \_\_\_\_\_ transducer.
- (15) Thermistors have \_\_\_\_\_ temperature co-efficient.
- (16) Give any two names of microphone.
- (17) How many types of logic circuits? Give its name.
- (18) What is the use of Flip-flop in digital electronics?
- (19) What is the use of IC 555 in digital electronics?
- (20) Draw the circuit diagram of J-K flip flop.

- 2 (a) Give any three answers in brief : 6
- (1) What is called multivibrator? Give its type.
  - (2) What is called clipper? Give the applications of clipping circuit.
  - (3) Explain the two transistor analogy of an SCR.
  - (4) Give the applications of differentiating circuit and integrating circuit.
  - (5) What is called thyristor? Give the applications of thyristor.
  - (6) Write short note: Burglar alarm using SCR.
- (b) Give any three answers : 9
- (1) Explain the working of combination clipper.
  - (2) What is called clamper? Explain positive clamper circuit.
  - (3) Explain a differentiating circuit.
  - (4) Write short note: DIAC.
  - (5) Explain automatic street light circuit using LDR and SCR.
  - (6) Explain automatic water level indicator using SCR.
- (c) Give any two answers in detail : 10
- (1) Explain construction and working of astable multivibrator with circuit diagram.
  - (2) Describe construction and working of monostable multivibrator.
  - (3) Explain the construction and characteristics of SCR.
  - (4) Describe the construction and characteristics of Triac.
  - (5) With the help of circuit diagram, explain illumination control using DIAC and Triac.

- 3** (a) Give any three answers in brief : **6**
- (1) What is called multiplexer? Write the applications of it.
  - (2) What is called Flip flop? Give its type.
  - (3) Write the scale of integration.
  - (4) Discuss Op-Amp as an inverting amplifier.
  - (5) Discuss the classification of transducers based on their application.
  - (6) Explain Piezoelectric transducers.
- (b) Give any three answers : **9**
- (1) Explain D- flip-flop with the circuit diagram and truth table.
  - (2) Write short note: Demultiplexer.
  - (3) Discuss Op-Amp as a summing amplifier.
  - (4) Explain how a transistor is fabricated in IC.
  - (5) Explain capacitive pressure transducer.
  - (6) Describe construction and working of thermocouple.
- (c) Give any two answers in detail : **10**
- (1) Explain R-S flip-flop with the circuit diagram and truth table.
  - (2) Explain multiplexer in detail with the circuit diagram and truth table.
  - (3) Explain LVDT in detail.
  - (4) Describe the fabrication of monolithic IC.
  - (5) Discuss the classification of ICs by structure.
-