



HDV-003-0493002

Seat No. _____

**B. Sc. / M. Sc. (Applied Physics)
(Sem. III) (CBCS) Examination**

November / December – 2017

**Applied Electronics : X
(New Course)**

Faculty Code : 003

Subject Code : 0493002

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Numbers in the right margin indicate marks.

- 1** Attempt any seven short questions : (two marks each) **14**
- (1) What is the "dark current" of photodiode?
 - (2) Draw the construction of solar cell.
 - (3) What is thermistor? Which materials are used to construct thermistor?
 - (4) Draw the general block diagram of voltage regulators.
 - (5) Sketch the block diagram of CRO.
 - (6) Draw symbol of FET and MOSFET.
 - (7) State the effect of V_{GS} on channel conductivity of n-channel JFET.
 - (8) Draw the basic flip-flop circuit using NOR gate.
 - (9) Which gates are the universal gates? Write name with proper symbol.
 - (10) Covert $(110110)_2$ into decimal.
- 2** (a) Write answers of any **two** : **10**
- (1) Draw the general structure of IR emitters and write the applications.
 - (2) Write the basic construction and characteristics of tunnel diode.
 - (3) Discuss photodiode with its applications.
 - (4) Describe basic operation of liquid crystal display.

- (b) Write answers of any **two** : **4**
- (1) Draw the symbol of given diodes.
 - (A) Schottky diodes
 - (B) Photo diodes
 - (C) Thermistor
 - (D) Tunnel diodes.
 - (2) What is photoconductive cell? Which materials are used for photoconductive cell?
 - (3) Discuss the application varicap (varactor) diode.
 - (4) Draw the construction and I-V characteristics of schottky diode.
- 3** (a) Write answers of any **two** : **10**
- (1) What is switching regulator? Draw the block diagram of three terminal voltage regulators.
 - (2) Explain theory and construction of Cathode Ray Tube.
 - (3) Explain shunt voltage regulation with basic shunt regulator circuit.
 - (4) Draw the block diagram of operation of delayed sweep.
- (b) Write answers of any **two** : **4**
- (1) What is Voltage regulation? Write the equation for voltage regulation.
 - (2) Draw the block diagram of series voltage regulator.
 - (3) What is Synchronization in CRO?
 - (4) Explain triggering in CRO.
- 4** (a) Write answers of any **two** : **10**
- (1) Give the difference between BJT and FET.
 - (2) Describe basic construction of a P-channel depletion type MOSFET.
 - (3) Explain fixed-bias configuration in FET.
 - (4) With help of neat circuit diagram explain the working of self bias method for FET.

(b) Write answers of any one : 4

(1) With the help of neat diagram write construction of n-channel FET.

(2) Explain voltage divider biasing in JFET.

5 (a) Write answers of any **two** : 10

(1) Explain AND, OR and NOT gates with truth table.

(2) Explain Master-Slave operation of a flip-flop.

(3) Design a 1-bit full adder with two half adders and minimum number of additional gates.

(4) Convert the following numbers as required in each case.

(1) $(25.625)_{10} = (?)_2$

(2) $(603.23)_{10} = (?)_2$

(b) Write answers of any **two** : 4

(1) What is binary half adder? Draw the circuit for it.

(2) Using K-map simplify

$$Y = A'BC + ABC + B'C + AC + A'B'C'$$

(3) Draw the circuit of a BCD adder using 4-bit binary adders.

(4) Use Boolean algebra to show that,

$$A'BC' + AB'C' + AB'C + ABC' + ABC = A+BC'$$
