



**HDY-003-1153003**

Seat No. \_\_\_\_\_

**M. Sc. (Electronics) (Sem. III) (CBCS) Examination**

**November / December – 2017**

**Paper - XI : OP-Amp & Its Applications**

**Faculty Code : 003**

**Subject Code : 1153003**

Time :  $2\frac{1}{2}$  Hours]

[Total Marks : 70

**1 Answer the following questions in brief : (any seven) 14**

- (1) Explain input bias and input offset currents.
- (2) Draw and explain equivalent circuit of an operational amplifier.
- (3) Define oscillator and multivibrator.
- (4) Design a narrow-band bandpass filter with  $F_C = 1$  kHz,  $Q=5$  and  $A_F=10$ .
- (5) Draw the block diagram of a typical operational amplifier and explain working of each in not more than 3 lines.
- (6) Mention advantages and disadvantages of active filters.
- (7) For an inverting amplifier designed using IC 741, with  $R_1 = 1$  k $\Omega$  and  $R_F = 4.7$ k $\Omega$ ; calculate values of  $A_F$ ,  $R_{iF}$ ,  $R_{oF}$ ,  $f_F$  and  $V_{oot}$ . ( $AOL = 200000$ ,  $R_i = 2$ M $\Omega$ ,  $R_o = 75$  $\Omega$ ,  $f_o = 5$ Hz)
- (8) Explain working of an op-amp integrator in brief.
- (9) Draw the circuit diagram of a closed loop differential amplifier. Also derive expression for its voltage gain.
- (10) Enlist characteristics of an ideal operational amplifier.

**2 Attempt any two of the following questions : (Each 7 Marks) 14**

- (1) With appropriate circuit diagram, explain any one application of instrumentation amplifier.
- (2) With necessary diagrams explain working of summing, scaling and averaging amplifier in inverting mode.
- (3) Write a detailed note on various open-loop configurations of an op-amp.

- 3** Answer the following questions :
- (1) Write a detailed note on RC-phase shift oscillator. **5**
  - (2) Explain use of instrumentation amplifier in temperature indicator and controller. **5**
  - (3) Explain AC amplifier with single power supply with help of necessary diagrams. **4**

**OR**

- 3** Answer the following questions :
- (1) Write a short note on floating load type voltage to current converter. **5**
  - (2) Write a detailed note on Schmitt Trigger. **5**
  - (3) Explain working principle of an oscillator. Also explain frequency stability. **4**
- 4** Answer the following questions :
- (1) What is slew rate? What are the causes? Explain effect of slew rate in real applications of op-amp. **5**
  - (2) Explain working of a square wave generator using op-amp. **5**
  - (3) Write a short note on peaking amplifier using op-amp. **4**
- 5** Answer any two of the following questions : (Each 7 Marks) **14**
- (1) Write a detailed note on variation in offset voltage due to change in power supply and temperature.
  - (2) For voltage series feedback derive expressions for closedloop voltage gain, input resistance, output resistance, bandwidth and total output offset voltage.
  - (3) Draw high frequency op-amp equivalent circuit and with help of necessary expressions, explain how open-loop gain varies with frequency.
  - (4) What is a filter? Explain design and working of first and second order low-pass filter. Design first and second order low-pass filter with  $F_c = 1000\text{Hz}$ .