



MBH-003-003203 Seat No. _____

B. C. A. (Sem. II) (CBCS) Examination

March / April - 2018

CS - 09 : Computer Organization & Architecture
(Old Course)

Faculty Code : 003

Subject Code : 003203

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

1 Answer the following : 20

- (1) A XOR gate has inputs A and B and output Y. Then the output equation is
- (2) Demorgan's theorem is
- (3) JK flip-flop is Universal flip-flop?
(True/False)
- (4) S-R type flip-flop can be converted into D type flip-flop if S is connected to R through
- (5) $J = 1, K = 1$ is a J-K flip-flop made to toggle?
(True/False)
- (6) An example of SOP expression is _____
- (7) On a Karnaugh map, grouping the 0s produces a
- (8) $1011001110 / 101 =$ _____
- (9) After Counting 00, 01, _____, 11.
- (10) SR flip-flops is face the indeterminate condition problem?
(True/False)
- (11) The Digital system usually operated on _____ system.
- (12) $110010101 * 1001 =$ _____
- (13) An encoder has $2n$ input lines and _____ output lines.
- (14) BR signal is activated by _____.

- (15) Logic states can only be _____ or 0.
- (16) IPO Stands for _____
- (17) DMA Stands for _____
- (18) Removing the CPU from the path and letting the peripheral device manage the memory buses directly is called _____.
- (19) Asynchronous counters are known as _____.
- (20) When CPU is executing the user programs then the CPU is said to be in _____.

2 (A) Attempt Any Three : 6

- (1) What is Boolean algebra?
- (2) What is Truth table?
- (3) What is Postulates?
- (4) What is Clock Pulses?
- (5) What is Combinational Circuit?
- (6) What is Sequential Circuit?

(B) Attempt Any Three : 9

- (1) Explain Boolean function using postulates.
- (2) Explain Universal Gate.
- (3) Explain Decoders
- (4) Explain Integrated Circuits.
- (5) Explain Block Diagram of Register.
- (6) What is Interrupt? Explain types of interrupts.

(C) Attempt Any Two : 10

- (1) Explain full-adder circuit in detail.
- (2) Write a short note on IC.
- (3) Explain Floating point representation.
- (4) Write a note on General Register Organization.
- (5) Write a note on DMAController.

- 3** (A) Attempt Any **Three** : **6**
- (1) Explain Major Component of CPU.
 - (2) What is register stack?
 - (3) What is memory stack?
 - (4) What is Polish Notation?
 - (5) Explain 2×4 decoders.
 - (6) What is mantissa and exponent?
- (B) Attempt Any **Three** : **9**
- (1) Explain major components of CPU.
 - (2) Explain binary counter.
 - (3) Explain Don't care condition
 - (4) Write a note on clocked D Flip-flop.
 - (5) Explain three variables Exclusive - OR gate.
 - (6) Explain NAND gate as Universal gate.
- (C) Attempt Any **Two** : **10**
- (1) Write a note on JK & T flip flop.
 - (2) Explain 3-bit Asynchronous Binary up Counter
 - (3) Explain in detail Block diagram of ALU
 - (4) What do you mean by Parity Bit? Describe how data is transferred using Parity Bit.
 - (5) Explain : Data Bus, Address Bus and Control lines.
-