



PBB-003-0493002 Seat No. _____

**B. Sc. / M. Sc. (Applied Physics) (Sem. III) (CBCS)
Examination**

November / December - 2018

**Applied Electronics : Paper - X
(New Course)**

Faculty Code : 003

Subject Code : 0493002

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory
(2) Numbers in the right margin indicate marks

- 1** Attempt any **seven** short questions : (Two marks each) **14**
- (1) Draw the symbol of given diodes
 - (a) Schottky diodes
 - (b) Photo diodes
 - (c) Thermistor
 - (d) Tunnel diodes.
 - (2) What are the essential differences between semiconductor diode and tunnel diode?
 - (3) What is photoconductive cell? Which materials are used for photoconductive cell?
 - (4) Draw the general block diagram of voltage regulators.
 - (5) What is Voltage regulation? Write the equation for voltage regulation.
 - (6) Sketch the block diagram of CRO.
 - (7) Write the Shockley's equation which relates the gate to source bias voltage and drain current in JFET.
 - (8) Give the name of different configurations of biasing in FET.
 - (9) Which gates are the universal gates? Write name with proper symbol.
 - (10) Write the advantages of digital systems compared to analog system.

- 2** (a) Write answers of any **two** : **10**
- (1) Explain varicap (varactor) diode with an application.
 - (2) Write the basic construction and characteristics of tunnel diode.
 - (3) Discuss photodiode with its applications.
 - (4) Explain solar cell with necessary figures and diagram.
- (b) Write answer of any **one** : **4**
- (1) Describe basic operation of liquid crystal display.
 - (2) Draw the general structure of IR emitters and write the applications.
- 3** (a) Write answers of any **two** : **10**
- (1) Explain theory and construction of Cathode Ray Tube.
 - (2) Describe Synchronization in CRO.
 - (3) Explain series voltage regulation with basic series regulator circuit
 - (4) Explain shunt voltage regulation with basic shunt regulator circuit.
- (b) Write answer of any **one** : **4**
- (1) Draw the block diagram of operation of delayed sweep.
 - (2) What is switching regulator? Draw the block diagram of three terminal voltage regulators.
- 4** (a) Write answers of any **two** : **10**
- (1) Describe basic operation of Enhancement type MOSFET.
 - (2) Explain Fixed-bias configuration in FET.
 - (3) Give the difference between BJT and FET
 - (4) Explain voltage divider biasing in FET.

- (b) Write answers of any **two** : 4
- (1) Sketch the basic construction of a P-channel depletion type MOSFET.
 - (2) Draw symbol of FET and MOSFET.
 - (3) State the effect of VGS on channel conductivity of n-channel JFET.
 - (4) Write at least two differences between JFET and MOSFET.

- 5** (a) Write answers of any **two** : **10**
- (1) Explain AND, OR and NOT gates with truth table.
 - (2) Explain Master-Slave operation of a flip-flop.
 - (3) Give the difference between combinational logic circuit and sequential logic circuit.
 - (4) Convert the following numbers as required in each case.
 - (i) $(1234)_{10} = (?)_2$
 - (ii) $(603.23)_{10} = (?)_2$

- (b) Write answer of any **one** : 4
- (1) What is binary half adder? Draw the circuit for it.
 - (2) Using K-map simplify the product sum form the function given by $F(A, B, C, D) = \pi M(0, 6, 10, 12)$
