



PBB-003-04950003 Seat No. _____

**B. Sc. / M. Sc. (Applied Physics) (Sem. V) (CBCS)
Examination**

November / December - 2018

**Advanced Electronics : Paper - XVIII
(New Course)**

Faculty Code : 003

Subject Code : 04950003

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory
(2) Figures on the right side indicate marks

- 1** Attempt any **seven** short questions (Two marks each) **14**
- (1) Which amplifiers are used for PA (Public Address) systems?
 - (2) What is meant by power transistors?
 - (3) Define PLL (Phase Locked Loop)
 - (4) Voltage buffer gives unity gain. Then why do we use it?
 - (5) Is it possible to have an ideal OPAMP in practice? Why?
 - (6) Why IC741 is called OPAMP?
 - (7) What is virtual ground?
 - (8) How current mirror circuit is used?
 - (9) What is meant by filter circuits?
 - (10) Explain Gain Bandwidth product for OPAMP.
- 2** (a) Write answers of any **two** : **10**
- (1) Differentiate Linear and non linear ICs.
 - (2) Discuss 555 time IC.
 - (3) Explain PLL with its application.
 - (4) Explain VCO.

- (b) Write answers of any **one** : 4
- (1) What is Astable multivibrator? Explain using 555 timer circuit.
 - (2) Explain differential amplifier.
- 3** (a) Write answers of any **two** : **10**
- (1) Discuss all types of Power Amplifiers in brief
 - (2) Differentiate Class A and Class B operations.
 - (3) Where are class C and Class D amplifiers used?
 - (4) Discuss power amplifier distortion and heat sinking.
- (b) Write answer of any **one** : 4
- (1) With proper sketches of load line, differentiate different class of power amplifiers.
 - (2) Explain class B push-pull arrangement.
- 4** (a) Write answers of any **two** : **10**
- (1) How OPAMP can be used in instrumentation? Explain with one example.
 - (2) Discuss OPAMP DC offset parameters.
 - (3) Discuss OPAMP as controlled source.
 - (4) Explain common mode and differential modes of OPAMP.
- (b) Write answer of any **one** : 4
- (1) Draw and explain circuit of OPAMP as differentiator.
 - (2) Draw and explain circuit of OPAMP as an inverting and non inverting amplifier.

- 5** (a) Write answers of any **two** : **10**
- (1) Explain in detail different types of filter circuits
 - (2) List and discuss ideal characteristics of OPAMP.
 - (3) Draw and explain circuit of OPAMP as an integrator.
 - (4) Draw and explain circuit of OPAMP as a summing amplifier
- (b) Write a short note of any **one** : **4**
- (1) Write short note on applications of OPAMP
 - (2) Define and explain slew rate and CMRR for 741 IC.
-