



MAO-003-001603

Seat No. _____

B. Sc. (Sem. VI) (CBCS) Examination

March / April - 2018

Physics : Paper - 603

(Solid State Electronics)

Faculty Code : 003

Subject Code : 001603

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All the questions are compulsory.
(2) Give answer of all questions in answer book only.
(3) Figures on the right indicate full marks.

1 Objective Questions : 20

- (1) A multivibrator which generates waves without any external triggering pulse is known as _____ multivibrator.
- (2) If a d.c or constant input is applied to differentiating circuit, the output will be _____.
- (3) A bidirectional avalanche diode is also known as _____.
- (4) When a transistor is driven to saturation, ideally the $I_c = \underline{\hspace{2cm}}$ and $V_{ce} = \underline{\hspace{2cm}}$.
- (5) The temperature sensing element thermistor has _____ temperature coefficient.
- (6) The angle at which the device is triggered is known as _____.
- (7) _____ can not fabricated in monolithic IC.
- (8) A TRIAC is a _____ layer device.
- (9) A device that convert energy in one form to energy in another form is known as _____.
- (10) In OPAMP as an integrator, the feedback component is _____.
- (11) When the input fed to differentiating circuit is a triangular wave, the output will be _____ wave.
- (12) In monolithic IC capacitor, the SiO_2 layer acts as _____.

- (13) A small portion of positive and negative half cycle of the signal can be removed with the help of _____ circuit.
- (14) Write full name of SCS.
- (15) Write full name of LASCR.
- (16) A microphone is classified as an _____ transducer.
- (17) A thermocouple is a _____ generating type transducer.
- (18) A tourmaline crystal represents _____ transducer.
- (19) Thermopiles are made by connecting thermocouples in _____.
- (20) An ideal OP-AMP has _____ voltage gain.

- 2** (a) Answer any **three** question : **6**
- (1) State the disadvantages of mechanical switch ?
 - (2) State the circuit symbol and forward biased characteristics of an SCR.
 - (3) State circuit symbol of any two thyristor.
 - (4) State the classification of ICs based on scale of integration.
 - (5) State any two photovoltaic transducer,
 - (6) State any two disadvantages of an IC.
- (b) Answer any **three** question : **9**
- (1) Explain in brief classification of transducer.
 - (2) Explain in brief switching action of a transistor.
 - (3) Explain in brief multivibrator.
 - (4) Explain in brief OP-AMP as an adder.
 - (5) Explain in brief inductive pressure transducer.
 - (6) Explain in brief multiplexer.
- (c) Answer any **two** question : **10**
- (1) Draw the V-I characteristic of an SCR and explain its working principle.
 - (2) With a neat circuit diagram, explain working of a monostable multivibrator.
 - (3) Explain the working of illumination control circuit using DIAC and TRIAC.
 - (4) Explain JK flip flop with circuit diagram and truth table.
 - (5) Explain OP-AMP as differentiator with circuit diagram.

- 3** (a) Answer any **three** question : **6**
- (1) What is demultiplexer ?
 - (2) Draw the circuit diagram of transistor mono stable multivibrator.
 - (3) Compare transistor and triac.
 - (4) State advantages of ICs.
 - (5) What is transducer ?
 - (6) What is flip-flop ?
- (b) Answer any **three** question : **9**
- (1) Explain in brief fabrication of resistor and capacitor in ICs.
 - (2) Explain the truth table of RS flip-flop.
 - (3) Explain in brief any one-rectifier circuit using SCR.
 - (4) Explain in brief fabrication of diode in ICs.
 - (5) Write a short note on OP-AMP as an integrator.
 - (6) Write a short note on TRIAC.
- (c) Answer any **two** question : **10**
- (1) Discuss classification of ICs by functions.
 - (2) Explain the working of automatic street light circuit using thyristor.
 - (3) With a neat circuit diagram, explain working of bi stable multivibrator.
 - (4) Explain the capacitive pressure transducer with diagram.
 - (5) Explain the combinational and sequential logic circuits.
-