



PAR-003-1015027 Seat No. _____

B. Sc. (Sem. V) (CBCS) Examination

October / November - 2018

Physics : 503

(New Course)

Faculty Code : 003

Subject Code : 1015027

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Symbols have their usual meanings.
(3) Figures to the right indicate marks.

- 1 (a) Answer the following in short : 4
- (1) Write the formula for power gain in dB.
 - (2) Which coupling method is used to amplify extremely low frequencies ?
 - (3) Define distortion in an amplifier.
 - (4) Give the units of thermal resistance.
- (b) Answer in brief : (any **one**) 2
- (1) A three stage amplifier has a first stage voltage gain of 50, second stage voltage gain of 100 and third stage voltage gain of 300. Find the total voltage gain in dB.
 - (2) A power transistor dissipates 4W. If the maximum junction temperature is 90°C, find the maximum ambient temperature at which it can be operated, given that $\theta=10^{\circ}\text{C}/\text{W}$.
- (c) Answer in detail : (any **one**) 3
- (1) Give the comparison of different types of coupling methods.
 - (2) Define performance quantities of power amplifiers.
- (d) Write notes on : (any **one**) 5
- (1) Explain R-C coupled amplifier with neat circuit diagram.
 - (2) Show that the maximum collector efficiency of transformer coupled class A amplifier is 50%.

- 2 (a) Answer the following in short : 4
- (1) Give the limitations of mechanical switch.
 - (2) Give the advantages of electronic switches.
 - (3) Define an integrating circuit.
 - (4) Define a clipping circuit.
- (b) Answer in brief : (any **one**) 2
- (1) An astable multivibrator has $R_2 = R_3 = 12\text{k}\Omega$ and $C_1 = C_2 = 0.02\mu\text{f}$. Find the time period and frequency of the output wave form.
 - (2) A peak-to-peak input voltage of 20V is applied to a positive clipper. If $R_L = 1\text{k}\Omega$ and $R = 200\Omega$, determine the output voltage for each half cycle.
- (c) Answer in detail : (any **one**) 3
- (1) Explain how a transistor works as a switch.
 - (2) Show that the output of a differentiating circuit is derivative of the input voltage.
- (d) Write notes on : (any **one**) 5
- (1) Explain astable multivibrator with neat circuit diagram.
 - (2) What do you understand by a clamping circuit? Explain the working of a negative clamper with a neat circuit diagram.
- 3 (a) Answer the following in short : 4
- (1) What is the need of regulated power supply ?
 - (2) Write the equation of voltage regulation.
 - (3) Define differential amplifier.
 - (4) Give the classification of ICs based on structure.
- (b) Answer in brief : (any **one**) 2
- (1) A power supply has a voltage regulation of 1%. If the no-load voltage is 30V, what is its full-load voltage?
 - (2) A non-inverting op-amp has $R_1 = 10\text{k}\Omega$ and $R_f = 1\text{M}\Omega$. Determine its voltage gain.
- (c) Answer in detail : (any **one**) 3
- (1) Explain transistor series voltage regulator.
 - (2) Write the characteristics of an ideal op-amp.

- (d) Write notes on : (any **one**) 5
- (1) Write a note on series feedback voltage regulator.
 - (2) Explain the use of op-amp as an adder.
- 4 (a) Answer the following in short : 4
- (1) Define transducers.
 - (2) Give two examples of nuclear transducers.
 - (3) Define tachometer.
 - (4) Write the equation which gives the relation between temperature and resistance of a metallic wire.
- (b) Answer in brief : (any **one**) 2
- (1) A platinum wire with $R_0 = 100\Omega$ and $\alpha = 0.00385$, is kept in an environment at 100°C . What is its resistance?
 - (2) A wire strain gauge with a gauge factor $K=5$ is bonded to an iron member which is subjected to a strain of 10^{-7} . If the original no-strain resistance of the gauge is 100Ω , calculate the change in gauge resistance.
- (c) Answer in detail : (any **one**) 3
- (1) Explain strain gauge.
 - (2) Explain resistive position transducer.
- (d) Write notes on : (any **one**) 5
- (1) Explain construction and working of LVDT.
 - (2) Write a note on thermistor.
- 5 (a) Answer the following in short : 4
- (1) Write the difference between electrical and electronic instruments.
 - (2) Give the advantages of a digital voltmeter.
 - (3) Define flip-flop.
 - (4) Write the logic equations of SUM and CARRY for half-adder.

- (b) Answer in brief : (any **one**) **2**
- (1) If $R_A = R_B = 47k\Omega$ and $C=1000$ pF, calculate the frequency of oscillation of astable 555 timer.
 - (2) Calculate the output pulse width for the 555 timer of monostable multivibrator given that $R_A = 4.7k\Omega$ and $C = 1.5 \mu f$.
- (c) Answer in detail : (any **one**) **3**
- (1) Write six applications of CRO.
 - (2) Write a note on demultiplexer.
- (d) Write notes on : (any **one**) **5**
- (1) Draw a block diagram of CRO and explain.
 - (2) Write a note on half-adder.
-