



PBU-1020

Seat No. _____

M. C. A. (Sem. I) (CBCS) Examination

December - 2018

P-1020 : Computer Organization and Architecture

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- 1 (a) Attempt the following : 4
- (1) Define : processor.
 - (2) 1024 MB = _____ KB
 - (3) What is MICR ?
 - (4) Convert decimal number 100 into equivalent binary number.
- (b) Attempt any **one** of the following : 2
- (1) Perform $(1011001.0011)_2 + (101.1111)_2$
 - (2) Convert $(1001010.11011)_2$ to equivalent decimal number
- (c) Attempt any **one** of the following : 3
- (1) Briefly explain touch screen
 - (2) What is scanner? Explain its mechanism in brief.
- (d) Attempt any **one** of the following : 5
- (1) Explain floating point representation in detail.
 - (2) How are integers stored in memory? Explain signed, unsigned, 1's complement and 2's complement integer representation using 4 bits.
- 2 (a) Attempt the following : 4
- (1) What is gate?
 - (2) Explain truth table.
 - (3) Explain product term.
 - (4) What is Boolean algebra?

- (b) Attempt any **one** of the following : **2**
- (1) Explain : NAND gate in brief.
 - (2) Explain exclusive or gate in brief.
- (c) Attempt any **one** of the following : **3**
- (1) Draw circuit diagram of OR gate using NAND gate.
 - (2) Draw circuit diagram of AND gate using NAND gate.
- (d) Attempt any **one** of the following : **5**
- (1) Explain circuit minimization using karnaugh map.
 - (2) Explain sum of product. Explain or gate with gate, truth table with sop and generate Boolean expression.
- 3** (a) Attempt the following : **4**
- (1) Define : Cache memory
 - (2) What is virtual memory ?
 - (3) Explain EPROM
 - (4) What is associative memory ?
- (b) Attempt any **one** of the following : **2**
- (1) Explain in brief : Instruction execution.
 - (2) Explain memory hierarchy in detail.
- (c) Attempt any **one** of the following : **3**
- (1) Explain architecture of PC with multiple types of buses.
 - (2) What is USB ? Explain in detail.

- (d) Attempt any **one** of the following : 5
- (1) What is ALU ? Explain in detail
 - (2) Define addressing mode. List and explain each addressing in detail.
- 4 (a) Attempt the following : 4
- (1) What is integrated circuit ?
 - (2) What is combinational circuit ?
 - (3) Which logical circuit converts n binary input data into 2_n input lines ?
 - (4) What is the use of arithmetic circuit ?
- (b) Attempt any **one** of the following : 2
- (1) Briefly explain half adder.
 - (2) Explain in brief : De-Multiplexer.
- (c) Attempt any **one** of the following : 3
- (1) What is comparator ? Explain it in detail.
 - (2) Differentiate : Encoder Vs Decoder.
- (d) Attempt any **one** of the following : 5
- (1) What is multiplexer? Explain it in detail with suitable example.
 - (2) What is binary adder/subtractor ? Explain in detail.
- 5 (a) Attempt the following : 4
- (1) Which flip flop is used to store the data in register ?
 - (2) Define : Registers
 - (3) Define : shift registers
 - (4) What is universal register ?
- (b) Attempt any **one** of the following : 2
- (1) Explain JK flip flop in brief.
 - (2) Draw graphical symbol and characteristic table for SR flip flop.

- (c) Attempt any **one** of the following : **3**
- (1) Briefly explain binary counter.
 - (2) Explain D Flip flop in brief.
- (d) Attempt any **one** of the following : **5**
- (1) What is a counter ? Differentiate Synchronous Vs Asynchronous counter
 - (2) Explain the storage registers with parallel input in detail.
-