



**PBA-003-1273001** Seat No. \_\_\_\_\_

**M. Sc. (ECI) (Sem. III) (CBCS) Examination**

**November / December - 2018**

**Paper - 9 : Advance Circuit & Network Concepts**  
*(New Syllabus)*

**Faculty Code : 003**

**Subject Code : 1273001**


Time :  $2\frac{1}{2}$  Hours]

[Total Marks : 70

- Instructions :** (1) Figures on right hand side indicate marks.  
(2) Assume suitable data if necessary.


**1** Answer the following : (Any Seven) **14**

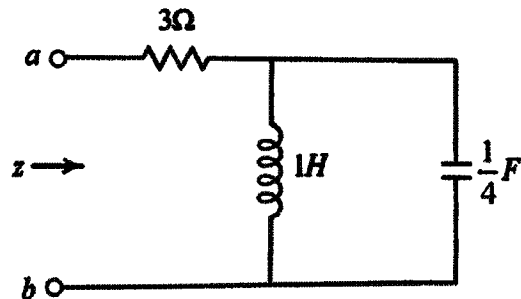- (1) Explain the "Translation in Frequency domain" property of Laplace Transform
- (2) Find Laplace Transform of  $(t + 2)^2 \cdot e^t$
- (3) Transform the circuit shown in fig. below to the s-domain & determine the Laplace Impedance



- (4) For the given denominator polynomial of a network function, verify the stability of the network by Routh criterion  $Q(s) = s^3 + 2s^2 + 8s + 10$
- (5) Define Step & Impulse signal. Draw waveform & write equation of both signals.

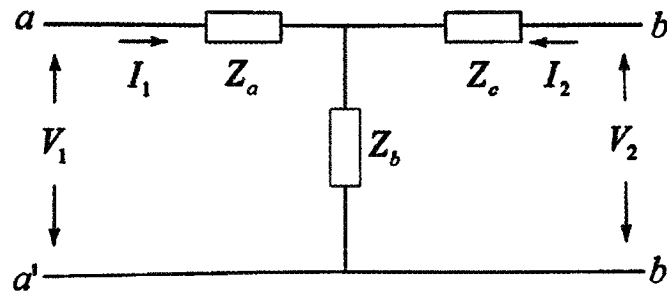
- (6) Derive  $Z_{11}$  and  $Z_{21}$  for the given circuit



- (7) Define Low Pass Filter & Band Pass Filter. Draw its attenuation characteristic.
- (8) Use initial & final value theorems to find the initial & final values of  $f(t)$  for following function :
- $$F(s) = \frac{4s^2 + 7s + 1}{s(s+1)^2}$$
- (9) Draw the T- and  $\pi$  - section circuit for constant k-type Low Pass Filter.
- (10) What is Attenuator & Equalizer? List different types of Attenuator & Equalizer.

**2** Answer the following : (Any Two)

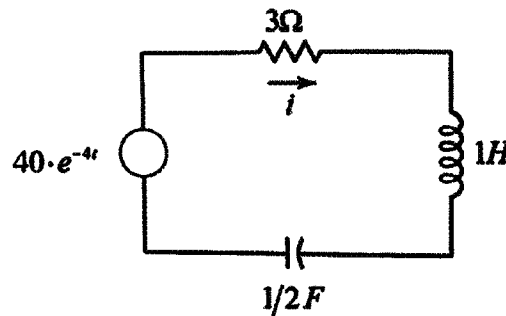
- (1) Determine the current 'i' if the circuit is driven by a 7 voltage source as shown in fig. below. The initial value of voltage across the capacitor & the initial current through the inductor both are zero.



- (2) Explain Lattice Phase Equalizer. 7
- (3) Derive different Y-parameters for a linear two port network. 7

3 Answer the following :

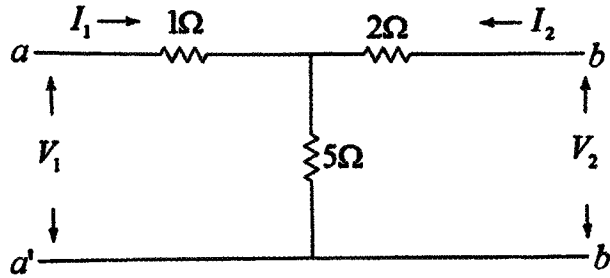- (1) Find the transmission parameters for circuit shown below 7



- (2) Explain Band Elimination Filter. 7

OR

3 Answer the following :

- (1) The driving point impedance of RL network is given as 7

$$Z(s) = \frac{5(s+1)(s+4)}{s(s+3) + (s+5)}$$

Determine Foster Form-1 for the network.


- (2) Derive equation for characteristic impedance,  $Z_{0T}$  7  
for T-network filter. Also prove that  $Z_{0T} = \sqrt{Z_{oc} \times Z_{sc}}$

4 Answer the following :

- (1) Derive ABCD parameters in terms of Z-parameters & Y-parameters. 7
- (2) Design k-type band pass filter having a design impedance of  $500\Omega$  and cut-off frequencies 1 KHz and 10 KHz. Also draw its circuit. 7

5 Answer the following : (Any Two)

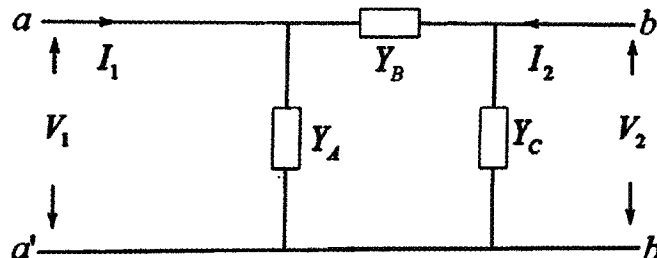- (1) Find short circuit admittance parameters for the circuit shown below 7



- (2) Explain natural response of RC circuit. 7
- (3) The driving point impedance of an LC network is 7  
given by  $Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$   
Determine 1<sup>st</sup> Cauer form of network.
- (4) Explain Bridged-T Attenuator. 7
-