



PBK-003-1271002 Seat No. _____

M. Sc. (ECI) (Sem. I) (CBCS) Examination

November / December - 2018

Foundation of Electronics : Paper - 2

(New Syllabus)

Faculty Code : 003

Subject Code : 1271002

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

Instructions :

- (1) Figures on right hand side indicate marks.
- (2) Assume suitable data if necessary.

1 Answer the following : (any seven) 14

- (1) Briefly explain mutual induction.
- (2) Write characteristics of a magnetic field of a circular coil.
- (3) Write about the basic properties of the charge.
- (4) Explain electric field intensity due to point charge.
- (5) Draw symbol of Resistor, Capacitor and Inductor.
- (6) Explain Coulomb's law.
- (7) Write about ideal voltage source.
- (8) Define volt and voltage.
- (9) Write an equation of total resistance of series and parallel combination.
- (10) Briefly explain Lorentz's force.

2 Answer the following : (any two)

- (1) Explain motional emf for a group of conductors. 7
- (2) Explain Kirchhoff's current and voltage laws with 7
determination of algebraic sign.
- (3) Explain following for AC waveform : 7
Amplitude, Frequency, Time Period, Peak Value.

- 3 Answer the following :
- (1) What is resistance ? Discuss resistance of a conductor. 5
 - (2) Briefly explain regarding intensity of electric field. 5
 - (3) Represent potential difference as negative of line integral. 4

OR

- 3 Answer the following :
- (1) Explain the voltage divider and current divider rule for resistive networks. 5
 - (2) Explain about different factors affecting the capacitance of a capacitor. 5
 - (3) Describe series and parallel combination of inductor. 4
- 4 Answer the following :
- (1) State the Ohm's law and discuss about series and parallel circuits. 7
 - (2) For a uniform electric field, prove the relation between E and V is $E = V/L$. 7
- 5 Answer the following : (any two)
- (1) Discuss the series and parallel connection of capacitors and derive the relevant formula for both types of connections. 7
 - (2) Assume that a current I flows in a circular coil. Prove that the magnetic field at the centre of the coil is $B = \frac{\mu_0 I}{2a}$ 7
 - (3) Derive the equations for the energy stored in a capacitor and inductor. 7
 - (4) Discuss the torque experienced by a current loop in a uniform magnetic field. 7