



MBH-003-003207 Seat No. _____

B. C. A. (Sem. II) (CBCS) Examination

March / April - 2018

CS - 09 : Comp. Organization & Architecture
(Old Course)

Faculty Code : 003

Subject Code : 003207

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

1 Attempt the following : 20

- (1) An inverter is also called a _____ gate.
- (2) NAND is complements of AND gate. True or false ?
- (3) The K-MAP is also known as _____ Diagram.
- (4) Which bus is Bi-Directional?
- (5) The Process of Inserting an Item into the stack is known as _____
- (6) Full Form of CPU.
- (7) Floating point representation is used to store _____
- (8) One byte = _____ bits
- (9) Full Form of VLSI.
- (10) Stack Means _____
- (11) Full form of SISO.
- (12) DMA stand for _____.
- (13) The Circuit used to store 1 bit of data is known as _____
- (14) Find 1's Complement 11010 = _____
- (15) If both input is high then what is output in NAND gate?
- (16) Which Combinational Circuit adds two Binary Bits?

- (17) Multiplication of 1101×100 is _____
- (18) What is Address Register in DMA Controller?
- (19) Division of $10110 \div 10$
- (20) _____ is a Digital Circuit having number of input lines and only one output line.

- 1 (A) Attempt any **three** out of six : **6**
- (1) Write a note on Encoder.
 - (2) Explain LSI, MSI, VLSI.
 - (3) Difference Between Combinational Circuit and Sequential Circuit.
 - (4) Explain Don't care Condition.
 - (5) Explain Binary Counter.
 - (6) Explain D Flip Flop.
- (B) Attempt any **three** out of six : **9**
- (1) What is Logic Gates? Explain AND, OR, NOT Gate with Example.
 - (2) What is K-MAP? Explain with Example.
 - (3) Write a Short Note on IC.
 - (4) Explain Floating Point Representation.
 - (5) Explain Stack Organization.
 - (6) Explain Bi-Directional Shift register.
- (C) Attempt any **two** out of five : **10**
- (1) Explain NAND Gate as Universal Gate.
 - (2) Explain S-R Flip Flop.
 - (3) Explain Full-Adder in Detail.
 - (4) Explain Input Output Processor.
 - (5) Explain Types of Interrupt.

- 3** (A) Attempt any **three** out of six : **6**
- (1) What is Parity Bit?
 - (2) List Advantages of Polish Notation.
 - (3) Explain Address Bus and Data Bus.
 - (4) Write the Terms (1) Truth table (2) Bus
 - (5) Perform Multiplication : $11011 * 110$
 - (6) Obtain 2's Complement : 101101
- (B) Attempt any **three** out of six : **9**
- (1) Explain ALU with Block Diagram.
 - (2) Explain Memory Bus.
 - (3) Explain types of Register.
 - (4) Explain De-Morgan's Theorems with truth table.
 - (5) Explain Error Detecting Codes.
 - (6) Explain Memory Stack.
- (C) Attempt any **two** out of five : **10**
- (1) Explain Control Word with Example.
 - (2) Explain Reverse Polish Notation.
 - (3) Explain $4 * 1$ Multiplexer.
 - (4) Explain Master-Slave Flip Flop.
 - (5) Explain DMA Controller.
-