



MBH-003-1032003 Seat No. _____

B. C. A. (Sem. II) (CBCS) Examination

March / April - 2018

CS - 09 : Computer Organization & Architecture
(New Course)

Faculty Code : 003

Subject Code : 1032003

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- 1 (A) Answer the Following : 4
- (1) A gate is a logic circuit with one or more input signals but _____ output signal.
 - (2) The Exclusive – NOR gate is equivalent to an _____ gate followed by an inverter.
 - (3) Demultiplexer is also known as _____
 - (4) A register is a group of _____ with each flip flop capable of storing one bit of information.
- (B) Answer any **one** in brief : 2
- (1) Explain SR Flip – Flop.
 - (2) Which are universal gates? Why?
- (C) Answer any **one** in detail : 3
- (1) Write a note on floating point representation.
 - (2) Explain combinational circuit.
- (D) Answer any **one** : 5
- (1) Explain General Register Organization.
 - (2) Explain ALU.

- 2 (A) Answer the Following : 4
- (1) Computer ICs work reliably because they are based on _____ design.
 - (2) PISO stands for _____
 - (3) BCD stands for _____
 - (4) $1011001110 \% 101 =$ _____
- (B) Answer any **one** in brief : 2
- (1) Draw the logic circuit for given Boolean Function.

$$F = (AB)(A + B' + C)(B'C')$$
 - (2) Write note on Control Word.
- (C) Answer any **one** in detail : 3
- (1) Simplify the following Boolean Function F together with the don't care condition.

$$F(W, X, Y, Z) = \sum(0, 1, 2, 3, 7, 8, 10)$$

$$D(W, X, Y, Z) = d(5, 6, 11, 15)$$
 - (2) Explain Shift Register.
- (D) Answer any **one** : 5
- (1) Explain 4×1 Multiplexer.
 - (2) Write a note on Boolean algebra.
- 3 (A) Answer the Following : 4
- (1) VLSI stands for _____
 - (2) $A + B * C$ prefix of it is _____
 - (3) Stack works on _____ Method.
 - (4) Software interrupt is initiated by _____
- (B) Answer any **one** in brief : 2
- (1) Obtain 1's and 2's complement
1110101
0011111110.
 - (2) Explain Don't care condition with example.

- (C) Answer any **one** in detail : **3**
- (1) Explain Demultiplexer.
 - (2) Explain Decoder.
- (D) Answer any **one** : **5**
- (1) State and prove De – Morgan's theorems.
 - (2) Explain Stack Organization
- 4 (A) Answer the Following : **4**
- (1) AND, OR and NOT are considered as universal gate (True / False).
 - (2) In Floating Point, the first part represents a signed, fixed – point number is called the mantissa (True / False).
 - (3) Stack Overflow is the example of Internal Interrupt. (True / False)
 - (4) Stack means last in first out (LIFO) (True / False).
- (B) Answer any **one** in brief : **2**
- (1) Multiply the binary numbers 1000 and 1001
 - (2) Divide 10001 by 110.
- (C) Answer any **one** in detail : **3**
- (1) Explain accumulator register.
 - (2) Explain stack organization.
- (D) Answer any **one** : **5**
- (1) Explain DMA Controller.
 - (2) Explain K – Map with example.

- 5 (A) Answer the Following : 4
- (1) ALU stands for _____
 - (2) DMA stands for _____
 - (3) The radix of binary number is _____
 - (4) _____ Flip – flops are free from race around problem.
- (B) Answer any **one** in brief : 2
- (1) What is Parity Bit?
 - (2) Define : Address Bus, Data Bus.
- (C) Answer any **one** in detail : 3
- (1) Explain ALU with Block diagram.
 - (2) Explain IOP.
- (D) Answer any **one** : 5
- (1) Explain Error Detecting Codes.
 - (2) Explain Bi – Directional Shift Register.
-