



PH-003-001603

Seat No. _____

B. Sc. (Sem. VI) (CBCS) Examination

July - 2018

Physics - 603

(Solid State Electronics)

(New Course)

Faculty Code : 003

Subject Code : 001603

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Digit on the right side indicate marks.
(3) Symbols have their usual meaning.

1 Answer the questions : 20

- (1) When a transistor is driven to saturation, ideally the output is _____ V.
- (2) _____ multivibrator is a square wave oscillator.
- (3) If transistor is used as a switch, and if $V_{CC} = 10 V$, $R_C = 1 K\Omega$ and $I_{CBO} = 10 \mu A$. when transistor is at cutoff, the value of V_{CE} near to _____ V.
- (4) When transistor (in CE arrangement) is in the cutoff region, the collector current is _____.
- (5) If 10 V dc is supplied to the input of differential circuit, its output will be _____.
- (6) For the integrating circuit, the capacitive reactance X_C should be _____ than the resistance R.
- (7) Input wave in integrating circuit is squarewave, its output will be _____.
- (8) For the regenerative action of SCR, the value of $(\alpha_1 + \alpha_2)$ should be near to _____.

- (9) The angle for which the device remains in conduction state is known as _____.
- (10) LDR is not a Thyristor. True or false?
- (11) For first quadrant characteristic of TRIAC, the terminal MT_1 is _____.
- (12) _____ cannot fabricated in monolithic IC.
- (13) An ideal OP-AMP is a _____ controlled device.
- (14) In inverting amplifier for OP-AMP, the feedback resistance R_f is $10 K\Omega$ and input resistance R_i is $1 K\Omega$, find the voltage gain.
- (15) In Op-Amp as differentiator, the feedback component is _____.
- (16) In Strain gauge, strain is directly proportional to change in _____.
- (17) In multiplexer, when $ABCD = 0000$, _____ data will be transmitted to output.
- (18) In J-K flip-flop, if both input is 1, the action is _____.
- (19) For flip-flop, outputs Q and \bar{Q} should be _____.
- (20) In SR flip-flop, if terminal S is '1', the action is called _____.

2 (A) Answer any **three** :

6

- (1) Write the advantages of electronics switches.
- (2) How transistor can be use as a switch ? Explain in brief.
- (3) In astable multivibrator, if $R_2 = R_3 = 10K\Omega$ and $C_1 = C_2 = 0.01 \mu F$. Determine the time period and frequency of the output squarewave.
- (4) Write down the list of the methods of triggering SCR.
- (5) What is firing angle and conduction angle?
- (6) Draw the circuit diagram of transistor astable multivibrator.
- (7) Draw the layer diagram, symbol and characteristic curve of DIAC.

(B) Answer any **three** : **9**

- (1) What is differentiating circuit ? Draw circuit diagram and prove the relation between output and input voltage.
- (2) What is clipping circuit? Explain biased clipper.
- (3) Explain multivibrator with proper block diagram.
- (4) Explain differentiating circuit.
- (5) Explain structure and operation of TRIAC.
- (6) Explain 'Off at dark' circuit.

(C) Answer any **two** : **10**

- (1) Explain transistor free running multivibrator.
- (2) Explain switching action of a transistor.
- (3) Explain two transistor analogy of SCR.
- (4) Explain application of DIAC–TRIAC as a static switch.
- (5) Discuss illumination control circuit using DIAC–TRIAC.

3 (A) Answer any **three** : **6**

- (1) What is an integrated circuit?
- (2) Write the disadvantages of monolithic ICs.
- (3) What is transducer? Explain it.
- (4) What is the basic principle of self-generating inductive transducer?
- (5) Draw logic diagram of basic RS flip–flop and realize the truth table.
- (6) Draw logic diagram and give truth table of JK flip–flop.

(B) Answer any **three** : **9**

- (1) What is an Op–Amp ? Explain.
- (2) Explain Op–Amp as Adder.
- (3) Explain Tachometer with proper diagram.
- (4) Write a note on thin film IC.
- (5) What is combinational and sequential logic circuits?
- (6) Discuss D–flip–flop.

(C) Answer any **two** : **10**

- (1) Explain use of Op–Amp as inverting amplifier.
 - (2) Explain strain gauge.
 - (3) Explain constructive and working of LVDT.
 - (4) Explain S–R flip flop with circuit diagram and realize truth table.
 - (5) Write a note on classification of transducer.
-