



PD-003-1203006

Seat No. _____

M. Sc. (Sem. III) (CBCS) Examination

June / July - 2018

ET - 4 : Physics

(Analog & Digital Systems)

Faculty Code : 003

Subject Code : 1203006

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Number on right margin indicates marks.

1 Attempt any seven : 14

- (a) Draw schematic symbol for the 8-pin op-amp and label each pin.
- (b) List the open-loop op-amp configurations. What do you mean by open-loop and closedloop op-amp configurations ?
- (c) Define feedback. What are the different types of feedback used in Op-Amp ?
- (d) Define filter. What are the different types of filters.
- (e) List the ideal op-amp electrical characteristics.
- (f) How many bits would you require if you want a resolution of at least 40 mV and the full scale range is 10 V ?
- (g) Prepare truth table for the Boolean function :
 $F = A + B' \cdot C$.
- (h) Write the BCD codes.
- (i) Which of the following counters can be operated at higher clock frequency ? Ripple counter and synchronous counter
- (j) Draw the circuit of 4-bit shift left register. How many clock pulses are required to store a 4-bit binary number serially ?

2 Answer the following : (any two)

- (a) Discuss designing steps of differential amplifier from two identical emitter - biased circuits. **7**

- (b) Define an operational amplifier. Draw block diagram of a typical op-amp and discuss function of each block. 7
- (c) Define following parameters : 7
- (i) CMRR
 - (ii) Slew rate
 - (iii) Power consumption
 - (iv) Output voltage swing.
- 3 (a) Derive necessary formulae for closed-loop voltage gain, input and output resistances with feedback in the case of voltage series feedback amplifier. 7
- (b) Draw and briefly discuss frequency responsive curves of active filters. 7
- OR**
- 3 (a) A binary full adder circuit has three inputs : X_n, Y_n and previous carry C_{n-1} and two outputs SUM and CARRY. The canonical Boolean expressions for outputs are : 7
- $$S_n (C_{n-1}, X_n, Y_n) = \sum (1, 2, 4, 7)$$
- $$C_n (C_{n-1}, X_n, Y_n) = \sum (3, 5, 6, 7)$$
- Design binary full adder circuit using all 2-input NAND gates.
- (b) Write a note on designing of BCD to Exces-3 code converter. 7
- 4 Attempt any **two** : 7
- (a) Draw the circuit of asynchronous Mode-8 counter and explain its operation with counting sequence and timing diagram. 7
 - (b) Explain the logic and operation of 8-bit successive Approximation ADC with neat diagrams. 7
 - (c) Write brief note on Ring counters. 7
- 5 Attempt any **two** : 14
- (a) Voltage follower
 - (b) Zero-crossing detector
 - (c) 4-Bit magnitude comparator
 - (d) Tracking ADC.