



RAH-003-001402

Seat No. _____

B. Sc. (Sem. IV) (CBCS) Examination

March / April – 2019

Physics : Paper - 401

(Optics, Laser & Electronics)

(Old Course)

Faculty Code : 003

Subject Code : 001402

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Symbols have their usual meaning.
(3) Figures right side indicate marks.

- 1 Answer all the following questions : (each one mark) **20**
- (1) Write formula for the radius of n^{th} half period zone.
 - (2) Write formula for the dispersive power of the prism.
 - (3) The rate of spontaneous transition $R_{sp} =$ _____.
 - (4) Ruby laser is a _____ laser.
 - (5) Give the name of excited states with longer life time.
 - (6) Multimode fibers are classified into _____ types.
 - (7) What is the equation of numerical aperture ?
 - (8) Write formula for the fraction Refractive index.
 - (9) How many types of basic transistor LC oscillators ?
 - (10) The condition $kA_v \geq 1$ is known as _____ criterion.
 - (11) The modulated radio-wave travels with the velocity _____ m/s.
 - (12) Microphone is device which converts sound waves into _____ waves.
 - (13) In AM-Modulation, Amplitude of _____ waves changed ?
 - (14) A modulated wave can be demodulated by _____ circuit.

- (15) JFET has _____ terminals semiconductor device.
- (16) Junction Field effect transistor (FET) is _____ control device.
- (17) NOR-Gate is combination of _____ gates.
- (18) Give the name of the universal gates.
- (19) In photo-transistor, write the equation of collector current ?
- (20) Solar Cell converts the solar energy into _____.

- 2** (a) Define the following : (answer any **three**) **6**
- (1) Plane diffraction Grating.
 - (2) Spontaneous emission.
 - (3) Pumping Process.
 - (4) Numerical Aperture (NA)
 - (5) Term : Feedback
 - (6) LC-Oscillators
- (b) Explain the following : (answer any **three**) **9**
- (1) Comparison between a zone plate and convex lens.
 - (2) Three level pumping scheme.
 - (3) Medical applications of fiber optics.
 - (4) Advantages of fiber optics.
 - (5) Principle and construction of Phase-shift oscillator.
 - (6) Principle and working of Colpitt oscillator.
- (c) Write answer any two : **10**
- (1) Explain the theory of zone plate.
 - (2) Derive the equations of Einstein relationships.
 - (3) Explain the construction and working of Ruby laser.
 - (4) Derive an expression for acceptance angle of the optical fiber.
 - (5) Explain the construction, working of Hartley Oscillator.

- 3** (a) Define the following : (answer any **three**) **6**
- (1) Modulation and its types.
 - (2) Amplitude modulation (AM).
 - (3) Advantages of JFET.
 - (4) Analog and Digital signal.
 - (5) OR-gate
 - (6) Light Dependent Resistance.
- (b) Explain the following : (answer any **three**) **9**
- (1) Essentials in demodulation.
 - (2) A.M. diode Detector.
 - (3) Give the symbol and construction of MOSFET.
 - (4) NOT-gate with necessary figure and truth table.
 - (5) NAND and NOR gate.
 - (6) Photo transistor.
 - (7) Construction and working Solar cell.
- (c) Write answer any **two** : **10**
- (1) Explain the transistor AM-modulator.
 - (2) Describe the construction and working of a UJT.
 - (3) Discuss, Encoders and Decoders in detail.
 - (4) Explain the Superhetrodyne Radio receiver.
 - (5) Describe in detail, the Liquid crystal display (LCD).
-