



**JAG-P-XVIII**

Seat No. \_\_\_\_\_

**B. Sc. / M. Sc. (Applied Physics) (Sem. V) (CBCS)  
Examination**

**November - 2019**

**Advanced Electronics : Paper - XVIII**

*(New Course)*

Time :  $2\frac{1}{2}$  Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.  
(2) Numbers in the right margin indicate marks.

- 1** Attempt any **seven** short questions : (two marks each) **14**
- (1) What is VCO ? Where do we use it ?
  - (2) What is the difference between virtual ground and real ground ?
  - (3) What is meant by Offset Null ?
  - (4) Define Phase Locked Loop (PLL).
  - (5) What is Unity gain circuit? When do we use it ?
  - (6) Which device is called Power Amplifier ?
  - (7) Why filters are required in electronic devices.
  - (8) Why IC741 is called OPAMP ?
  - (9) What is Gain Bandwidth Product ?
  - (10) Explain how current mirror circuits are used.
- 2** (a) Write answers of any **two** : **10**
- (1) Explain OPAMP as an Integrator.
  - (2) Explain OPAMP as a differentiator
  - (3) Explain class -B PUSH -PULL arrangement.
  - (4) How OPAMP can be useful in instrumentation ?
- (b) Write answer of any **one** : **4**
- (1) Why power amplifiers are classified in different CLASS type ? What is the role of load line ?
  - (2) Why heat sinks are used in power amplification ?

- 3 (a) Write answers of any **two** : 10
- (1) Differentiate Linear and Non Linear Ics
  - (2) Explain 555 timer operation.
  - (3) Explain 555 as multivibrator.
  - (4) Explain the term VCO and its functioning.
- (b) Write answer of any **one** : 4
- (1) Differentiate Class A and Class B operation.
  - (2) Which amplifier is used for Public address system (PA system) ?
- 4 (a) Write answers of any **two** : 10
- (1) Discuss OPAMP as an inverting amplifier and Non inverting amplifier.
  - (2) List the characteristics of Ideal OPAMP.
  - (3) OPAMP is widely used. List down main uses of OPAMP.
  - (4) Discuss OPAMP as an averaging and summing amplifier.
- (b) Write answers of any **two** : 4
- (1) Discuss OPAMP working for AC and DC signals.
  - (2) Discuss OPAMP DC Offset parameter.
- 5 (a) Write answers of any **two** : 10
- (1) Differentiate Low pass and High Pass Filters.
  - (2) Explain Cutoff frequency concept and Pass band for each type of filters.
  - (3) Explain OPAMP as a controlled Voltage Source.
  - (4) Explain OPAMP as a controlled Current source.
- (b) Write answer of any **one** : 4
- (1) Draw and explain pin diagram of OPAMP IC741.
  - (2) Explain Differential amplifier with reference to OPAMP.
-