



JAR-003-1271004 Seat No. _____

M. Sc. (ECI) (Sem. I) (CBCS) Examination

December - 2019

**Introduction To Electronics Devices
And Circuits : Paper - IV**

Faculty Code : 003

Subject Code : 1271004

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

1 Answer the following : (Any Seven out of Ten) 14

- (1) If $a = 0.98$ for CE NPN transistor, what will be the value of β
- (2) List the different types of filters that are used in rectifier circuit.
- (3) List the different method to fabricate Diode.
- (4) Give the difference between an ordinary transistor and FET. (2 points each)
- (5) What is PIN diode?
- (6) Which types of transformer is used in following rectifiers?
 - (A) Half wave Rectifier
 - (B) Full wave Rectifier
- (7) What is an IDEAL diode? Draw its characteristic graph.
- (8) For given BJT $I_B = 10 \mu A$ and $\beta = 99$. Calculate I_C , I_E and a .
- (9) Draw the Symbol for ENHANCEMENT P – CHANNEL MOSFET and N – CHANNEL JFET.
- (10) The energy gap in Insulator is _____ while in Semiconductor it is _____.

- 2** Answer the following : (Any **Two** out of Three) **14**
- (1) Write a note on an Extrinsic semiconductor and explain how P type and N type semiconductors are formed.
 - (2) Explain in detail the construction, biasing and application of ZENER diode.
 - (3) What do you mean by Filter circuit in rectifier? Explain all filters in detail.
- 3** Answer the following : **14**
- (1) Explain TUNNEL diode in detail. Show TUNNELING effect using energy band gap theory.
 - (2) What is PN diode junction capacitance? Write about VARACTOR diode and its applications.
- OR**
- 3** Answer the following : **14**
- (1) What do you mean by MOSFET? Explain it with necessary diagrams.
 - (2) Which are the different 2 ports parameters? Explain Hybrid model and its parameters in detail.
- 4** Answer the following : **14**
- (1) What is DC rectifier? Explain WHEATSTONE BRIDGE rectifier circuit in detail.
 - (2) Explain PN junction diode with its different biasing and V-I characteristics.
- 5** Answer the following : (Any **Two** out of Four) **14**
- (1) What is Transistor? Explain CE mode with suitable circuit and V-I characteristics.
 - (2) Explain SCHOTTKY diode in detail. Write the difference between Schottky diode and PN diode.
 - (3) Explain following terms for Semiconductor.
 - (A) Doping
 - (B) Charge carriers
 - (C) Donor
 - (D) Acceptor
 - (E) Intrinsic semiconductor

- (4) For a: given circuit, Find
- (1) Output voltage
 - (2) Current through Zener diode
 - (3) Voltage drop across R_s
 - (4) Load current

[$R_S = 5K\Omega$, $R_L = 10K\Omega$, $V_Z = 50V$ and source voltage is (V_s) $120V$]

