



JAH-003-1275003

Seat No. _____

M. Sc. (ECI) (Sem. V) (CBCS) Examination

November - 2019

Advance Instrumentation : Paper - XIX
(New Course)

Faculty Code : 003

Subject Code : 1275003

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions carry equal marks.
(2) Figures on right hand side indicate marks.

- 1 (a) State whether the following statements are true or false : 8
- (1) Wave analyzers are used in the low RF range below 50 MHz and down through the AF range.
 - (2) The output power Wattmeter is designed to directly measure the output power in an arbitrary load.
 - (3) The overall efficiency of coils and capacitors intended for RF applications is best evaluated using the Q value.
 - (4) Magger is used to measure very high resistance.
 - (5) A wheatstone bridge may be used to measure the ac resistance of various types of wires.
 - (6) Maxwell's bridge measures an unknown inductance in terms of a known capacitor.
 - (7) Impedances at AF or RF are commonly determined by means of a dc Wheatstone bridge.
 - (8) The strain gauge is an example of an active transducer.

- (b) Answer the following : (any **three**) **6**
- (1) Define the term transducer.
 - (2) Give the abbreviation of LVDT recorder.
 - (3) List five physical quantities that transducer measures.
 - (4) What is the difference between an indicator and recorder?
- 2** Answer the following : (any **two**)
- (1) Draw and discuss the basic wave analyzer. **7**
 - (2) What is difference between a wave analyzer and a harmonic distortion analyzer? Draw the circuit diagram and explain the working of a heterodyne type wave analyzer. **7**
 - (3) Explain the working principle of an output power meter. **7**
- 3** Answer the following :
- (1) What is LCR Bridge? How can L, C and R be measured using a skeleton LCR bridge? **5**
 - (2) Discuss the principle applications of Kelvin's bridge. Also describe the operation of a Kelvin's bridge. **5**
 - (3) Describe the operation of the Wheatstone bridge. **4**
- OR**
- 3** Answer the following :
- (1) Give the types of recorders in detail. **5**
 - (2) What are the basic components of a Magnetic recorder? Explain its operation. **5**
 - (3) Give the advantages and disadvantages of Digital data recording. **4**

- 4 Answer the following :
- (1) List the different types of transducers. Explain Piezu electrical transducer. 5
 - (2) What is a signal conditioner? What are the basic elements of a single conditioner? 5
 - (3) Draw and discuss the cavity wave meter. 4
- 5 Answer the following : (any two)
- (1) Give the classification of electronic recording instruments. Discuss about Strip chart recorder. 7
 - (2) Explain the principle of operation of a stroboscope. Also explain how the speed of a motor can be measured using a stroboscope. 7
 - (3) What is an op.amp? Give the electrical characteristics of an ideal op.amp. Also discuss the integrator circuit using operational amplifier with diagram. 7
 - (4) What are the requirements of a dummy load? Discuss about Bolometer and method of power measurement. 7
-