



PR-003-1154001

Seat No. _____

M. Sc. (Electronics) (Sem. IV) (CBCS) Examination

August - 2020

Automation With PLC & SCADA : Paper - 13
(New Course)

Faculty Code : 003

Subject Code : 1154001

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions carry equal marks.
(2) Figures on right hand side indicate marks.

1 Answer the following : (Any Seven) 14

- (1) Give the full name of PLC and SCADA.
- (2) Enlist the PLC applications.
- (3) Write any four reference designators used in PLC.
- (4) Draw NAND and NOR ladder logic diagram.
- (5) Define multiprocessing.
- (6) What is the purpose of the control transformer in machine control system ?
- (7) Draw symbols of selector switch and indicator lamp.
- (8) Draw an electrical symbols of transformer and limit switch.
- (9) Explain pushbutton switch in brief.
- (10) What is purpose of the fuse in control transformer?

2 Answer the following : (Any Two)

- (1) Define machine control terminology. **7**
- (2) Write a note on relays and delay on timer. **7**
- (3) Explain types of memory of the PLC. **7**

- 3** Answer the following :
- (1) Write a note on fundamental of ladder logic diagram. **7**
 - (2) Write in detailed on any data handling ladder logic function. **7**

OR

- 3** Answer the following :
- (1) Write a short note on bit data files. **7**
 - (2) Explain in detail comparison instruction. **7**

- 4** Answer the following :
- (1) Explain XIC, XIO and OTE instructions with its symbol. **7**
 - (2) Draw and describe output latch and unlatch instructions of PLC. **7**

- 5** Answer the following : (Any **Two**)
- (1) Explain in detail one-shot rising instruction. **7**
 - (2) Draw an electrical and ladder logic diagram of the AND-OR logic. Explain each in brief. **7**
 - (3) Draw PLC architecture diagram and explain executive memory in brief. **7**
 - (4) Draw and describe basic operation of the PLC. **7**
