



PW-003-1204006

Seat No. _____

M. Sc. (Sem. IV) Examination

August - 2020

ET - 10 : Physics

(Pulse & Microwave Electronics)

(New Course)

Faculty Code : 003

Subject Code : 1204006

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :**
- (1) All questions are compulsory.
 - (2) Number on right margin indicates marks.

- 1 Attempt any seven : 14**
- (a) Define antenna. What are the different types of antenna ?
 - (b) Define isotropic antenna and non-resonant antenna.
 - (c) Define RADAR. Write a full form of RADAR.
 - (d) List the applications of microwaves in various fields.
 - (e) List the name of microwave tubes and solid state microwave devices.
 - (f) Define : Duty cycle for a rectangular waveform. Calculate duty cycle of a rectangular waveform of frequency 1 kHz and pulse width 500 micro-second.
 - (g) Draw the functional block diagram of timer IC 555.
 - (h) Define fractional tilt for a square waveform.
 - (i) Draw the circuit of IC 555 - Astable multi-vibrator.
 - (j) Draw RC integrating circuit for best integration of input square wave for frequency 10 kHz.
- 2 Attempt any two : 7**
- (a) Derive criteria for getting good differentiation and integration of a periodic waveform. Design RC differentiating circuit to produce the best spikes of frequency 1 kHz. 7
 - (b) Derive expression to relate 'rise time' and 'fall time' of input waveform to upper cut-off frequency and lower cut-off frequency of an amplifier, respectively. 7
 - (c) Write a detailed note on biased clipping and clamping circuits. 7

- 3 (a) Draw the circuit of IC 555 monostable multi-vibrator and explain its operation and designing. 7
- (b) Sketch the circuit of Schmitt trigger using transistors. Design the circuit for the following specifications : 7
 UTP = 5 Volts, transistor $\beta=100$, $I_c = 2\text{mA}$, supply voltage $V_{cc} = 12$ volts, speed up capacitor maximum value = 36 pF.
- OR**
- 3 (a) Draw and label block diagram of pulsed radar system and discuss its working principle in detail. 7
- (b) Derive necessary equation for maximum range of radar (r_{max}). 7
- 4 Attempt any **two** : 7
- (a) Draw schematic diagram of two-cavity Klystron amplifier and discuss its operation with applegate diagram. 7
- (b) Discuss in detail : Antenna with parabolic reflector. 7
- (c) Discuss following display methods 7
 Automatic target and moving target indication.
- 5 Attempt any **two** : 14
- (a) Reflex Klystron
- (b) Gunn diode
- (c) RC Ramp waveform generator
- (d) Transistorized astable multivibrator.
-