



BCH-003-1015027

Seat No. _____

B. Sc. (Sem. V) (W.E.F. 2016) Examination

August - 2021

503 - Physics

(Solid State Electronics)

(New Course)

Faculty Code : 003

Subject Code : 1015027

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :**
- (1) Symbols and notations have their usual meaning.
 - (2) Total marks of the question is indicated on the right side of the question.
 - (3) Attempt any five questions out of the following ten questions.

- 1 (a) Answer the following questions in short : 4
- (1) What is a multistage amplifier ?
 - (2) 1 bel = _____ dB.
 - (3) The output stage of multistage amplifier is also called _____.
 - (4) Class-C amplifiers are used as _____.
- (b) Answer the following question in brief : 2
- Draw the neat diagram of push-pull amplifier.
- (c) Answer the following questions in detail. 3
- Explain Thermal Runaway.
- (d) Write note on : 5
- Explain Push-pull amplifier.
- 2 (a) Answer the following questions in short : 4
- (1) Define biased clipper circuit.
 - (2) Define astable multivibrator.
 - (3) Bistable multivibrator is also known as _____.
 - (4) Clipper circuit is also known as _____.
- (b) Answer the following questions in short. 2
- A peak-to-peak input voltage of 20 V is applied to a positive clipper, determine output voltage for each half cycle.
- ($R_L = 1 \text{ k}\Omega$ and $R = 200 \Omega$)

- (c) Answer the following question in detail. 3
Give the basic difference among three multivibrator.
- (d) Answer the following question in detail : 5
Draw the neat circuit diagram of an astable multivibrator and explain its working.
- 3** (a) Answer the following in short : 4
(1) Zener diode can be used as _____.
(2) Write the equation for voltage regulation.
(3) What is DC Power supply ?
(4) Zener diode is operated in _____ region.
- (b) Answer the following question in brief. 2
A power supply has a voltage regulation of 1%. If the no-load voltage is 30V, what is the full load voltage ?
- (c) Answer the following question in detail. 3
Explain transistor series voltage regulator.
- (d) Write note on : 5
Explain the zener diode as a voltage regulator.
- 4** (a) Answer the following question in short : 4
(1) Define Op-Amp.
(2) What indicates the (+) and (-) sign in Op-Amp. ?
(3) The Op-Amp is a _____ controlled device.
(4) Where an Op-Amp is basically used ?
- (b) Answer the following question in brief : 2
Explain : Common mode and differential mode signals.
- (c) Answer the following question in detail : 3
Explain : Adder or summing amplifier.
- (d) Write note on : 5
Explain : Inverting amplifier and Non-inverting amplifier.
- 5** (a) Answer the following questions in short : 4
(1) Strain gauge is a _____ Transducer.
(2) LVDT is a _____ inductive transducer.
(3) A transducer is device that _____ energy in one form to energy another form.
(4) A microphone is an example of _____ transducer.
- (b) Answer the following question, in brief. 2
What is transducer ? Explain it.
- (c) Answer the following question in detail. 3
Explain strain gauge.
- (d) Write note on : 5
Explain construction and working of LVDT.

- 6 (a) Answer the following questions in short. 4
 (1) Write full form of CRO and CRT.
 (2) What is a rectifier type AC meter ?
 (3) Define : Multimeter.
 (4) Give the types of multimeter
- (b) Answer the following question in brief : 2
 Explain full-wave rectifier.
- (c) Answer the following question in detail. 3
 Mention application of CRO.
- (d) Answer the following question in detail. 5
 Explain the CRO.
- 7 (a) Answer the following questions in short. 4
 (1) For D.C., capacitor having a _____ resistance.
 (2) Write the equation of total gain of a multistage amplifier.
 (3) Class _____ power amplifier has the highest collector efficiency.
 (4) Class _____ operation gives the maximum distortion.
- (b) Answer the following question in brief. 2
 Give the circuit diagram for transformer coupled amplifier.
- (c) Answer the following question in detail. 3
 Explain frequency response of R-C coupled amplifier.
- (d) Write note on : 5
 Explain transformer coupled amplifier with neat circuit diagram.
- 8 (a) Answer the following questions in short. 4
 (1) Define a switching circuit.
 (2) The multivibrator 100% positive feedback is applied. True or False ?
 (3) The positive clipper removes the positive half cycle of the input voltage. True or False ?
 (4) If the input to a differentiator circuit is a saw-tooth wave, the output wave will be _____.
- (b) Answer the following question in brief : 2
 Define the switching circuit and mention its essential parts.

- (c) Answer the following question in detail. 3
 Explain how a transistor works as switch.
- (d) Write note on : 5
 What is a clipper circuit ? Explain the working of positive clipper with and without bias applied.
- 9** (a) Answer the following questions in short. 4
 (1) Thermistors have _____ temperature coefficient of resistance.
 (2) Write the definition of transducer.
 (3) Write the equation of gauge factor.
 (4) Write the principle of capacitive pressure transducer.
- (b) Answer the following question in short. 2
 A wire strain gauge with a gauge factor $K = 5$ is bonded to a iron member which is subject to a strain of 10^{-7} . If original no-strain resistance of the gauge is 100Ω calculate the change in gauge factor $K = 5$.
- (c) Answer the following question in detail. 3
 Explain capacitive pressure transducer.
- (d) Answer the following question in detail. 5
 Describe the carbon microphone.
- 10** (a) Answer the following questions in short. 4
 (1) Flip-flop can be used as a _____ device in computer.
 (2) IC 74147 is used for _____ purpose.
 (3) Decimal number 786 is convert into BCD.
 (4) The output of a clock circuit is _____.
- (b) Answer the following question in brief. 2
 Determine the output pulse width for the monostable 555 timer, when $R_A = 20 \text{ K}\Omega$ and $C = 0.1 \mu F$
- (c) Answer the following question in detail. 3
 Draw logic diagram and give truth table of JK flip-flop and explain in brief.
- (d) Write note on : 5
 Draw the neat circuit diagram at an astable multivibrator using IC-555 and obtain the expression for its frequency.