



BBH-003-001603 Seat No. _____

B. Sc. (Sem. VI) (CBCS) Examination

July – 2021

Physics : Paper-603

(Solid State Electronics)

(Old Course)

Faculty Code : 003

Subject Code : 001603

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

Instructions :

- (1) Attempt all questions.
- (2) Figures to the right indicate marks.
- (3) Notations have their usual meaning.

1 Fill in the blank with proper answer : **20**

- (1) Bistable multivibrator is also known as _____.
- (2) A circuit that can ON and OFF power to an electrical circuit is known as _____ circuit.
- (3) The multivibrator which generates square wave of its own is known as _____.
- (4) Full form of SCR is _____.
- (5) An SCR has _____ pn junctions.
- (6) A DIAC has _____ terminals.
- (7) Full form of LDR is _____.
- (8) The LDR responds to _____.
- (9) A thyristor can be used as a _____.
- (10) The ideal open loop gain of an Op-Amp is _____.
- (11) In small scale integration, component density is _____.
- (12) The band width of an ideal Op-Amp is _____.
- (13) LVDT has one primary but _____ secondary coils.
- (14) Microphone is an _____ transducer.
- (15) A _____ is a most widely sensor used to measure the temperature.

- (16) Flip-flop can be used as a _____ device in computer.
- (17) _____ Flip-flop has only one input.
- (18) A circuit with many inputs but one output is called _____.
- (19) A circuit with only one input but many outputs is called _____.
- (20) When the rectangular wave is applied at the input to an integrating circuit, the output wave will be a _____ wave.

- 2** (a) Answer any **three** : **6**
- (1) Define multivibrator and explain its working principle.
 - (2) Define electro-mechanical switch and write its advantages.
 - (3) Write the applications of clipping circuits.
 - (4) What is thyristor ?
 - (5) Explain firing angle.
 - (6) Explain voltage triggering of thyristor.
- (b) Answer any **three** : **9**
- (1) Explain differentiating circuit.
 - (2) Explain how transistor works as switch.
 - (3) Explain two transistor analogy of SCR.
 - (4) Write applications of thyristors.
 - (5) Write a note on DIAC.
 - (6) Draw only circuit diagram of temperature control circuit.
- (c) Answer any two in detail : **10**
- (1) Explain working of monostable multivibrator with neat circuit diagram.
 - (2) What is clipper circuit ? Explain the working of negative clipper with and without bias applied.
 - (3) Explain construction, working and characteristic of an SCR.
 - (4) Write a note on TRIAC.
 - (5) Explain illumination control circuit using DIAC and TRIAC.

- 3** (a) Answer any **three** : **6**
- (1) What is an IC ?
 - (2) Define CMRR and explain its importance.
 - (3) What is transducer ?
 - (4) Write the advantages of LVDT.
 - (5) Explain sequential circuit.
 - (6) Write the applications of multiplexer.
- (b) Answer any three : **9**
- (1) Write the advantages of ICs.
 - (2) Explain Op-Amp as comparator.
 - (3) Explain strain gauge.
 - (4) Explain resistive position transducer.
 - (5) Discuss on D flip-flop.
 - (6) Write a note on multiplexer.
- (c) Answer any two in detail : **10**
- (1) Explain the classification of ICs based on structure.
 - (2) Explain Op-Amp as an adder.
 - (3) Explain construction and working of LVDT.
 - (4) Write a note on piezoelectric transducer.
 - (5) Write a note on J-K flip-flop.
-