



BBA-003-1154001

Seat No. _____

M. Sc. (CBCS) (Sem. IV) Examination

July - 2021

Electronics : Paper - 13

(Automation with PLC & SCADA) (New Course)

Faculty Code : 003

Subject Code : 1154001

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) Answer any five out of ten questions.
(2) Figures on right hand side indicate marks.

1 Answer the following. **14**

- (1) Define PLC.
- (2) What is a shoe box PLC?
- (3) Draw and explain ground test circuit.
- (4) What types of memory might a PLC contain?
- (5) What is a two-hand operation of PLC?
- (6) What is the purpose of the control transformer in control system?
- (7) What is the purpose of programing unit?

2 Answer the following. **14**

- (1) Draw the NAND gate ladder logic diagram.
- (2) What is meaning of TR, F, PB and SS in PLC?
- (3) List the name of PLC input and output devices.
- (4) Draw basic framework diagram of the PLC.
- (5) Give full form of given reference designators.
 - OL
 - CB
 - M
 - L
- (6) List four types of I/O modules?
- (7) What is the purpose of the shrouded pushbutton actuator?

- 3 Answer the Following. 14
(1) Write a note on delay-off and delay-on timer relay.
(2) Draw and explain control transformer and fuse of the ladder diagram.
- 4 Answer the Following. 14
(1) Write a note on pushbutton and pushbutton actuator switches.
(2) Draw and describe Relays.
- 5 Answer the Following. 14
(1) Draw and explain following switches in brief.
• Limit switch
• Selector switch
• Mushroom head switch
(2) Draw and discuss an anti-tie down and anti-repeat operation of machine control.
- 6 Answer the following. 14
(1) Draw and write about AND-OR and OR-AND logic circuit diagram with appropriate ladder logic diagram.
(2) Draw and explain system block diagram of the PLC.
- 7 Answer the following. 14
(1) Write a note on latching contacts and explain with its suitable diagram.
(2) Draw and explain single cycle operation of machine.
- 8 Answer the following. 14
(1) Explain various types of machine control terminology.
(2) Write a note on majority circuit with suitable example.
- 9 Answer the following. 14
(1) Write a note on oscillator circuit in the PLC.
(2) Draw and explain R-S flip flop.
- 10 Answer the following. 14
(1) Write a note D flip flop and T flip-flop.
(2) Draw wiring diagram and programing rung diagram for AND-OR logic.