



DBY-003-1032003

Seat No. _____

B. C. A. (Sem. II) (CBCS) (W.E.F. 2016) Examination

July - 2022

CS-09 : Computer Organization & Architecture

Faculty Code : 003

Subject Code : 1032003

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Each question has equal Mark.

- 1 (a) Attempt following questions : 4
(1) An Inverter is also called ___ gate.
(2) What is Truth Table ?
(3) Define Universal Gate ?
(4) Define Ex-OR gate.
- (b) Answer in brief : (Any One) 2
(1) Define Full Adder.
(2) Define NOT gate with Truth Table.
- (c) Answer in detail : (Any One) 3
(1) Explain Don't care Condition with K-Map.
(2) Explain AND Gate & OR gate with Truth table.
- (d) Write a note on : (Any One) 5
(1) Explain SR-Flip Flop in details.
(2) Explain Combinational Circuit in detail.
- 2 (a) Attempt following questions : 4
(1) IC Stands for ____.
(2) What is Multiplexer ?
(3) What is Encoder ?
(4) A Demultiplexer is known as a data distributor.
(True/False)

- (b) Answer in brief : (Any One) 2
- (1) Define Parallel Register.
 - (2) Define 4-bits Binary Counter.
- (c) Answer in detail : (Any One) 3
- (1) Explain Block Diagram of Register.
 - (2) Explain Decoders (3x8)
- (d) Write a note on : (Any One) 5
- (1) Explain Multiplexer (4x1).
 - (2) Explain IC in detail.
- 3 (a) Attempt following questions : 4
- (1) In which method Stack Works ?
 - (2) What is Parity Bit ?
 - (3) A four bit number is given 1001. Its 1's complement is ____.
 - (4) Radix of the Binary Number is ____.
- (b) Answer in brief : (Any One) 2
- (1) Multiply 1101 by 110.
 - (2) Divide 1010 By 11.
- (c) Answer in detail : (Any One) 3
- (1) Divide 101101 By 110.
 - (2) Explain floating point representation.
- (d) Write a note on : (Any One) 5
- (1) Explain Fixed Point Representation.
 - (2) Explain Error detecting code using parity bit.
- 4 (a) Attempt following questions : 4
- (1) Full form of CPU ____.
 - (2) Full form of ALU.
 - (3) Stack means last-in, First-out (LIFO) ? [True/False]
 - (4) Full form of RPN ____.

- (b) Answer in brief : (Any One) **2**
 (1) Define Memory Stack.
 (2) Define Register Stack.
- (c) Answer in detail : (Any One) **3**
 (1) Explain Block Diagram of ALU.
 (2) Explain Accumulator Register.
- (d) Write a note on : (Any One) **5**
 (1) Explain Major Components of CPU.
 (2) Explain Interrupts with their types.
- 5** (a) Attempt following questions : **4**
 (1) Full form of DMA ____.
 (2) Full form of IOP ____.
 (3) Data Bus is bi directional ? [True/False]
 (4) BR Signal is activated by DMA controller.
 [True/False]
- (b) Answer in brief : (Any One) **2**
 (1) What is Memory Bus ?
 (2) What is Address Bus ?
- (c) Answer in detail : (Any One) **3**
 (1) Explain Input-Output Buses.
 (2) Define Control lines with data bus.
- (d) Write a note on : (Any One) **5**
 (1) Explain DMA Controller in detail.
 (2) Explain Input Out Processor (IOP).
-