



**DBL-003-1015027**

Seat No. \_\_\_\_\_

**B. Sc. (Physics) (Sem. V) Examination**

**June - 2022**

**P-503 : Solid State Electronics**

*(Old Course)*

**Faculty Code : 003**

**Subject Code : 1015027**

Time :  $2\frac{1}{2}$  Hours]

[Total Marks : **70**

- Instructions :**
- (1) Symbols and notations have their usual meaning.
  - (2) Total marks of the question is indicated on the right side of the question.
  - (3) Attempt any five questions out of the following ten.

- 1** (a) Answer the following questions in short: **4**
- (1) 1 bel = \_\_\_\_\_ dB.
  - (2) Coupling capacitor is also known as \_\_\_\_\_.
  - (3) When the band width (BW) is multiplied by the gain at mid frequencies, gain band width (GBW) is obtained. (True / False)
  - (4) TC coupled amplifier is use for amplify low frequency signals. (True / False)
- (b) Answer the following question : **2**
- A two stage amplifier has a first stage voltage gain of 100, and second stage voltage gain of 200. Find the total voltage gain in dB.
- (c) Explain frequency response of R–C coupled amplifier. **3**
- (d) Write a short note on the role of capacitors in transistors amplifier. **5**
- 2** (a) Give answer in very short : **4**
- (1) Power amplifier is meant to decrease the power level of the input signal. (True / False)
  - (2) In the voltage amplifier transistor with high  $\beta$  is used in the circuit. (True / False)
  - (3) The change of output wave shape from the input wave shape of an amplifier is known as \_\_\_\_\_.
  - (4) The unit of thermal resistance ( $\theta$ ) is \_\_\_\_\_.

- (b) A power amplifier supplies 50W to an  $8\Omega$  speaker find : 2
- ac output voltage
  - ac output current.
- (c) Explain thermal runaway. 3
- (d) Give the classification of power amplifier and explain in brief. 5
- 3 (a) Give the answers in very short : 4
- A circuit that can turn ON and OFF power to an electrical circuit is called \_\_\_\_\_.
  - The transistor in saturation and cutoff states behaves as a switch. (True / False)
  - A multivibrator that continually changes its states without external triggering is known as \_\_\_\_\_ multivibrator.
  - In monostable multivibrator the width of duration of pulse at the collector of either transistor is given by  $T=R_2C_1$ .
- (b) An astable multivibrator having  $R_1 = R_2 = 12\text{ K}\Omega$  and  $C_1 = C_2 = 0.02\text{ }\mu\text{F}$ . Find the time period and frequency of the output wave forms. 2
- (c) Explain a differential circuit. 3
- (d) Draw the neat circuit diagram of an astable multivibrator and explain its working. 5
- 4 (a) Give answer in short : 4
- The minimum Load resistance.  
 $R_{L(\min)} = V_{FL} \times I_{FL}$  (true / false)
  - The Zener diode in voltage regulation must operate in the breakdown region. (True / False)
  - In transistor series voltage regulator output voltage is given by  $V_{\text{out}} = V_z - V_{BE}$ . (True / False)
  - In transistor shunt voltage regulator output voltage is equal to the \_\_\_\_\_.
- (b) A negative shunt clipper made with  $1\text{ K}\Omega$  resistance and  $3\text{ K}\Omega$  load resistance, is applied with an input having peak voltage +10V. Find the peak output voltage. 2
- (c) Explain how a transistor works as switch. 3
- (d) Explain in detail biased clippers. 5

- 5 (a) Give answer in short : 4
- (1) An integrated circuit (IC) is also known as \_\_\_\_\_.
  - (2) The first IC was developed by \_\_\_\_\_
  - (3) The IC is not repairable. (True / False)
  - (4) In large scale of integration (LSI) component density is \_\_\_\_\_.
- (b) Explain the basic idea of clamper. 2
- (c) Explain the type of voltage regulators. 3
- (d) Explain the Zener diode as a voltage regulator. 5
- 6 (a) Give answer in short : 4
- (1) Draw symbol of operational amplifier.
  - (2) What is the full form of CMRR ?
  - (3) For ideal op-amp the open-loop gain  $A_v$  is \_\_\_\_\_
  - (4) The adder circuit gives an output voltage equal to the algebraic sum of two or more input voltage. (True / False)
- (b) If the dc output voltage is 400 V with no-load attached to power supply but decreases to 300 V at full load, find the percentage voltage regulation. 2
- (c) Explain ordinary dc power supply. 3
- (d) Write note on series voltage regulator. 5
- 7 (a) Give answer in short : 4
- (1) \_\_\_\_\_ is device that converts energy in one form to the another form.
  - (2) Technometer is a device which converts \_\_\_\_\_ into an electrical signal.
  - (3) Give full form of LVDT.
  - (4) Strain gauge is \_\_\_\_\_ transducer.
- (b) Explain common mode and differential mode signals. 2
- (c) Explain : Op-Amp as unity follower. 3
- (d) Derive an expression for the output voltage of an Op-amp differentiator. 5
- 8 (a) Give answer in short : 4
- (1) Thermistor is the short form for \_\_\_\_\_
  - (2) What is the full form of RTD ?
  - (3) Gauge Factor (K) defined as the fractional ratio of the change in resistance to the change in length. True / False.
  - (4) Quartz crystal is used for high frequencies in crystal microphone. True/False

- (b) If  $R_1 = 10 \text{ K}\Omega$ ,  $R_f = 100 \text{ K}\Omega$ ,  $V_1 = 5\text{V}$  and  $V_2 = 6\text{V}$ , find the output voltage for the op-amp subtractor circuit. **2**
- (c) Explain resistance temperature detector. **3**
- (d) Explain construction and working of LVDT. **5**
- 9** (a) Give answer in short : **4**
- (1) The deflection type of instruments are analog instruments. (True / False)
- (2) The multimeter is also known as \_\_\_\_\_.
- (3) What is the full form of VTVM ?
- (4) Give the full form of CRO.
- (b) Describe the three ways of making measurements. **2**
- (c) Explain analog and digital instruments. **3**
- (d) Explain DVM with proper block diagram. **5**
- 10** (a) Write answer in short : **4**
- (1) If Half-Adder the output of the Ex-OR gate is called \_\_\_\_\_.
- (2) Multiplexer is also called \_\_\_\_\_
- (3) In NIBBLE MULTIPLEXER when SELECT is high, the right nibble is select to the output. (True / False)
- (4) BCD is an abbreviation for \_\_\_\_\_
- (b) Determine the frequency of oscillation for the astable 555 timer. Circuit specifications are  $R_A = R_B = 47 \text{ K}\Omega$  and  $C = 1000 \text{ PF}$ . **2**
- (c) Explain R/S flip-flop with the circuit diagram and truth-table. **3**
- (d) Write a note on multiplexer and demultiplexer. **5**
-