



DBZ-003-0492006 Seat No. _____

**B. Sc. / M. Sc. (Applied Physics) (Sem. III) (CBCS)
Examination**

July - 2022

**Basic Electronics : Paper-VIII
(New Course)**

Faculty Code : 003

Subject Code : 0492006

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions are compulsory.
(2) Numbers in the right margin indicate marks.

1 Attempt any SEVEN short questions : (Two marks each) **14**

- (1) Define intrinsic and extrinsic semiconductor.
- (2) What is the function of diode in rectifier ?
- (3) Draw the circuit diagram of optoisolator.
- (4) Give the application of CB, CE, CC amplifier.
- (5) Why collector is wider than emitter and base ?
- (6) Why is potential divider method of biasing became universal?
- (7) Write the input and output phase relation in CE, CB, CC circuit.
- (8) Draw the schematic symbol of LED and Zener diode.
- (9) Write the potential barrier voltage for Si and Ge.
- (10) Define PIV.

2 (A) Write answer of any **two** : (Five marks each) **10**

- (1) Derive an expression for the efficiency of a half wave rectifier.

- (2) What do you understand by intrinsic and extrinsic semiconductor?
- (3) Discuss the behavior of pn junction under forward and reverse biasing.
- (4) Describe transistor action in detail.
- 2 (B) Write answers of any one : 04**
- (1) Describe in detail the energy band in semiconductor.
- (2) Discuss the effect of temperature on semiconductor.
- 3 (A) Write answers of any two : (Five marks each) 10**
- (1) Explain the stability factor in voltage divider method.
- (2) Write short note on fixed bias for transistor and its effect on stability.
- (3) Explain the working of transformer coupled transistor amplifier with neat circuit diagram.
- (4) Write short note on Varactor diode.
- 3 (B) Write answers of any one : 04**
- (1) Explain the zener diode as voltage stabilizer.
- (2) Write the advantage and disadvantage of half wave and centre tap full wave rectifier.
- 4 (A) Write answers of any two : (Five marks each) 10**
- (1) Explain the working of LED and write its applications.
- (2) Explain the V-I characteristics of tunnel diode with tunnelling effect.
- (3) What do you understand by class A, class B, class C power amplifier ?
- (4) Write the operation and characteristic of photodiode.
- 4 (B) Write a short note on any one : 04**
- (1) Define α , Show that it is always less than unity.
- (2) Describe various region in CE transistor configuration of transistor working.

5 (A) Write answers of any **two** : (**Five** marks each) **10**

- (1) Explain the working of Full wave bridge rectifier with well labelled diagram.
- (2) Derive an expression for collector current (I_c) in CE connection.
- (3) Explain the input and output characteristics of CB connection.
- (4) Describe the potential divider method with suitable diagram.

5 (B) Write answers of any **one** : **04**

- (1) Give two applications of photodiode.
 - (2) Draw well labelled diagram of npn and pnp transistor and write its description.
-