



DBZ-003-1152004

Seat No. _____

M. Sc. (Electronics) (Sem. II) (CBCS) Examination

July - 2022

Advanced Digital Electronics : Paper-8

(New Course)

Faculty Code : 003

Subject Code : 1152004

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

- Instructions :** (1) All questions carry equal marks.
(2) Figures on right hand side indicate marks.

1 Answer the following : (Any seven) 14

- (1) What is digital electronics?
- (2) Draw logic circuit diagram of half subtractor.
- (3) What is a flip-flop?
- (4) What is a sequential and combinational logic circuits?
- (5) Draw logic circuit diagram of half adder.
- (6) What is a decoder? Explain in brief.
- (7) Explain magnitude comparator with suitable example.
- (8) Draw logic circuit diagram for given Boolean expression.
• $Y = \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot C$
- (9) What is the difference between latch and flip flop?
- (10) What is an ALU?

2 Answer the Following : (Any two) 14

- (1) Draw the logic diagram of a three-digit BCD adder and briefly describe its functional principle.
- (2) Draw and explain full-adder with suitable diagram.
- (3) Draw and describe full-subtractor logic circuit diagram.

- 3 Answer the following : 14
- (1) Write a note on controlled inverter.
 - (2) Explain J-K flip-flop with preset and clear inputs.

OR

- 3 Answer the following : 14
- (1) Differentiate encoder and priority encoder with its suitable diagram.
 - (2) Explain 4 to 1 and 8 to 1 multiplexer with its truth table.

- 4 Answer the following : 14
- (1) Briefly describe the concept of look-ahead carry generation with respect to its Use in adder circuits. What is its significance while implementing hardware for addition of binary numbers of longer lengths?
 - (2) Write a note on cascading magnitude comparator.

- 5 Answer the following : 14
- (1) Draw and explain D flip-flop and D latch.
 - (2) Draw and explain R-S flip-flop with active low inputs.
 - (3) Draw and explain 4*4 multiplier.
 - (4) Write a note on demultiplexer.
