



Seat No. _____

HAL-003-2015027

B. Sc. (Sem. V) (CBCS) Examination

June - 2023

Physics : 503

(New Course)

Faculty Code : 003

Subject Code : 2015027

Time : $2\frac{1}{2}$ / Total Marks : 70

Instructions :

- (1) All questions are compulsory.
- (2) Symbols have their usual meanings.
- (3) Figures to the right indicate marks.

- 1 (a) Answer the following in short : 4
- (1) Define band width of an amplifier.
 - (2) Write the function of emitter bypass capacitor.
 - (3) Define distortion in an amplifier.
 - (4) To which class does the push pull amplifier belong ?
- (b) Answer in brief : (any one) 2
- (1) Find the voltage gain in dB if the voltage gain is 40.
 - (2) A power transistor dissipates 7W. If the maximum junction temperature is 85°C , find the maximum ambient temperature at which it can be operated, given that $\theta = 6.5^{\circ}\text{C/W}$.
- (c) Answer in detail : (any one) 3
- (1) Give the comparison of different types of coupling methods.
 - (2) Write a note on thermal runaway.
- (d) Write notes on : (any one) 5
- (1) Explain transformer coupled amplifier with neat circuit diagram.
 - (2) Write a note on Push-pull amplifier.

- 2 (a) Answer the following in short : 4
- (1) Define astable multivibrator.
 - (2) Give two advantages of electronic switches.
 - (3) What is the other name for bistable multivibrator ?
 - (4) Define a clamping circuit.
- (b) Answer in brief : (any one) 2
- (1) An astable multivibrator has $R_2=R_3=15\text{k}\Omega$ and $C_1=C_2=0.05\ \mu\text{f}$. Find the time period and frequency of the output wave form.
 - (2) A peak-to-peak input voltage of 30V is applied to a positive clipper. If $R_L = 2.5\ \text{k}\Omega$ and $R = 220\Omega$, determine the output voltage for each half cycle.
- (c) Answer in detail : (any one) 3
- (1) Write the conditions necessary for an RC circuit to work as integrating circuit.
 - (2) Show that the output of a differentiating circuit is derivative of the input voltage.
- (d) Write notes on : (any one) 5
- (1) Explain monostable multivibrator with neat circuit diagram.
 - (2) What do you understand by clipping circuit ? Explain the working of a combination clipper with a neat circuit diagram.
- 3 (a) Answer the following in short : 4
- (1) What is the need of regulated power supply ?
 - (2) Write the equation of minimum load resistance.
 - (3) Define differential amplifier.
 - (4) Write the full form of VLSI.
- (b) Answer in brief : (any one) 2
- (1) A power supply has a voltage regulation of 1.5%. If the no-load voltage is 23V, what is its full-load voltage ?
 - (2) A non-inverting op-amp has $R_1 = 12\ \text{k}\Omega$ and $R_f = 1.3\ \text{m}\Omega$. Determine its voltage gain.
- (c) Answer in detail : (any one) 3
- (1) Explain voltage regulation.
 - (2) Write the characteristics of an ideal op-amp.
- (d) Write notes on : (any one) 5
- (1) Write a note on series feedback voltage regulator.
 - (2) Explain single ended input operation of a differential amplifier.

- 4 (a) Answer the following in short : 4
- (1) Define resonance time of thermistors.
 - (2) Give two examples of acoustical transducers.
 - (3) Write the principle of capacitive pressure transducer.
 - (4) Write the equation which gives the relation between temperature and resistance of a metallic wire.
- (b) Answer in brief : (any one) 2
- (1) A platinum wire with $R_0 = 75 \Omega$ and $\alpha = 0.004$, is kept in an environment at 90°C . What is its resistance ?
 - (2) A wire strain gauge with a gauge factor $K=3$ is bonded to a steel member which is subjected to a strain of 10^{-7} . If the original no-strain resistance of the gauge is 85Ω . Calculate the change in gauge resistance.
- (c) Answer in detail : (any one) 3
- (1) Explain strain gauge.
 - (2) Explain the working of tachometer.
- (d) Write notes on : (any one) 5
- (1) Explain construction and working of LVDT.
 - (2) Write a note on moving coil microphone.
- 5 (a) Answer the following in short : 4
- (1) Write the function of electron gun in CRT.
 - (2) Give the advantages of a digital voltmeter.
 - (3) Define flip-flop.
 - (4) Write the logic equations of SUM and CARRY for half-adder.
- (b) Answer in brief : (any one) 2
- (1) If $R_A=R_B=50 \text{ k}\Omega$ and $C=950 \text{ pF}$, calculate the frequency of oscillation of astable 555 timer.
 - (2) Calculate the output pulse width for the 555 timer of monostable multivibrator given that $R_A = 8 \text{ k}\Omega$ and $C=22 \mu\text{F}$.
- (c) Answer in detail : (any one) 3
- (1) Describe various functions of instruments.
 - (2) Write a note on encoder.
- (d) Write notes on : (any one) 5
- (1) Explain frequency determination using CRO.
 - (2) Write a note on D flip flop.