



Seat No. _____

H AJ-003-1153003

M. Sc. (Sem.-III) Examination

May - 2023

Electronics : Paper-11

(OP AMP & Its Application)

Faculty Code : 003

Subject Code : 1153003

Time : $2\frac{1}{2}$ Hours / Total Marks : 70

1 Answer the following: (Any 7 out of 10) **14**

- (1) Enlist the Ideal characteristics of an Op Amp.
- (2) Differentiate between Harmonic oscillators and Relaxation oscillators.
- (3) Draw the pin diagram of LM741.
- (4) List the advantages of an integrated circuit.
- (5) Show the classification of ICs based on Applications.
- (6) Differentiate between- Positive and negative feedback.
- (7) Explain Barkhausen criteria for oscillation.
- (8) What is Quadrature oscillator? Explain in brief.
- (9) For inverting op amp, if the circuit has $R_1 = 1k \Omega$, $R_f = 100 k \Omega$ and $V_{in} = 20mV$, Calculate its output voltage and gain.
- (10) Explain Different working' mode of IC 555 in brief.

2 Answer the following: (Any 2 out of 3) **14**

- (1) Draw the basic block diagram. of an Op Amp and explain each block in detail.
- (2) Write detailed note on voltage series feedback.
- (3) How can we use Op amp as voltage to Current converter? Show its applications. (at least 3)

3 Answer the following: 14

(1) Write a note on RC phase shift oscillator. Design it for $f_o = 250$ Hz.


(2) Draw the circuit and explain First order high pass filter.

Design first order low pass filter at a cutoff frequency of 1 kHz with a pass band gain of 2.


OR

3 Answer the following: 14

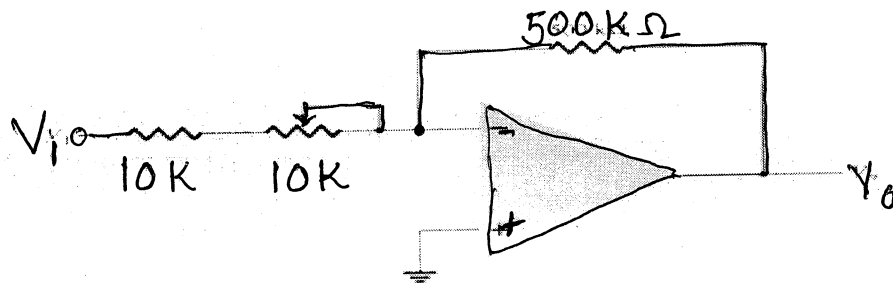(1) What is the output voltage range if $V_1 = 40$ mV ?



(2) Calculate the output voltage.

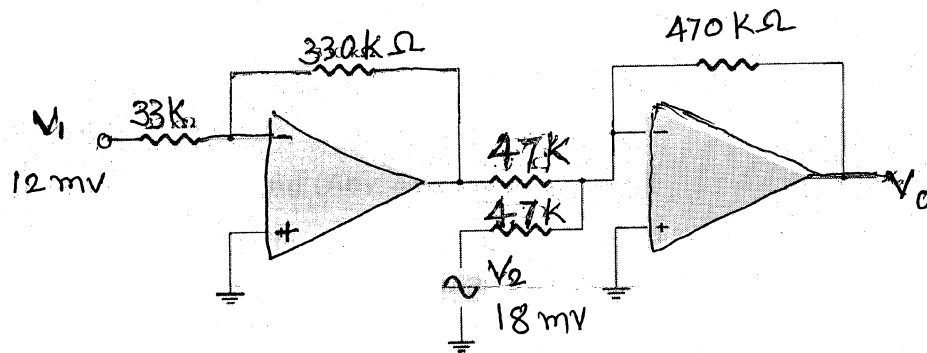

4 Answer the following: 14

(1) Draw proper diagram and explain Astable mode of IC 555.

Determine the value of capacitor C needed using $R_A = R_B = 7.5$ k Ω for operation at 350 kHz.

(2) Show OP Amp as summing, Scaling and averaging amplifier in Inverting mode.

5 Answer the following: (Any 2 out of 4)

14

- (1) Discuss DC offset: parameters of an OP AMP in the closed loop.
 - (2) Show how we use OP Amp as an integrator? Explain its modification for practical use.
 - (3) Discuss transducer bridge instrumentation amplifier and derive its output voltage.
 - (4) Explain any ONE application of LM565 in detail with necessary circuit.
-