



Seat No. \_\_\_\_\_

**HD-003-1204006**

**M. Sc. (Physics) (Sem. IV) (CBCS) Examination**

**April - 2023**

**ET-10 : Pulse & Microwave Electronics**

**Faculty Code : 003**

**Subject Code : 1204006**

Time :  $2\frac{1}{2}$  Hours / Total Marks : 70

- Instructions :** (1) All questions are compulsory.  
(2) Numbers in the right margin indicate marks.

- 1** Attempt any seven : **14**
- (a) Draw the circuit of double diode series noise clipper.
  - (b) Calculate duty cycle of a rectangular waveform of frequency 10 kHz and pulse width 50 micro second.
  - (c) A  $100 \mu F$  capacitor is charged to 10 V. It starts discharging through  $R = 100 k\Omega$  resistance. What will be the voltage across it at  $t = 0.693 RC$  ?
  - (d) Define rise time of pulse waveform. Show that for a step voltage input applied to RC circuit, the rise time  $t_r$  of the output is  $2.2 RC$ .
  - (e) Sketch the internal circuit diagram of timer IC-555.
  - (f) Define antenna.
  - (g) Write full form of RADAR. What are the basic functions of Radar ?
  - (h) List display methods used in Radar system.
  - (i) Give a list of linear beam microwave tubes.
  - (j) What do you mean by isotropic antenna and directional antenna ?

- 2 Attempt any **two** :
- (a) Draw and explain the operation of circuits of positive and negative biased clampers using diodes. 7
  - (b) Derive criteria for getting good differentiation and integration of a periodic waveform by RC circuit. Design integrating circuit for obtaining good integration of an input square wave of frequency 100 kHz. 7
  - (c) Define rise time and fractional tilt for a pulse waveform and derive expressions for relationship between rise time and upper cutoff frequency and fraction tilt and lower cut-off frequency of an amplifier. 7
- 3 (a) Draw the circuit of monostable multivibrator using transistors, explain its operation with necessary diagrams. 7
- (b) Sketch the circuit of Schmitt trigger using transistors and explain its working with input and output characteristics in detail. Draw the transfer characteristic of Schmitt trigger for  $LTP = 3\text{ V}$  and  $UTP = 5\text{ V}$ . 7
- OR**
- 3 (a) Derive Radar range equation. Discuss in detail the factors influencing maximum range of radar. Why "ground hopping" is emphasized for military air crafts ? 7
- (b) Discuss any two display methods of radar, in detail. What do you mean by blind speed.? An MTI radar operates at 10 GHz with pulse repetition frequency of 3000 pps. Calculate its lowest blind speed. 7
- 4 Attempt any **two** :
- (a) What are the different types of antennas ? Discuss any three types of antenna in detail. 7
  - (b) Discuss with neat diagrams construction and working of two cavity klystron. 7
  - (c) Discuss in detail how radiation pattern of antenna is generated ? What do you mean by "null zone" ? 7

**5** Attempt any **two** :

**14**

- (a) Discuss with circuit diagram's transistorized RC Ramp waveform generator in detail.
  - (b) Sketch the circuit of astable multivibrator using IC-555 and explain its operation.
  - (c) Write a detailed note with appropriate sketches on Yagi-Uda antenna. List its applications. Why is it called "super gain" antenna ?
  - (d) Draw a functional block diagram of a pulsed radar system and describe the function of each block.
-